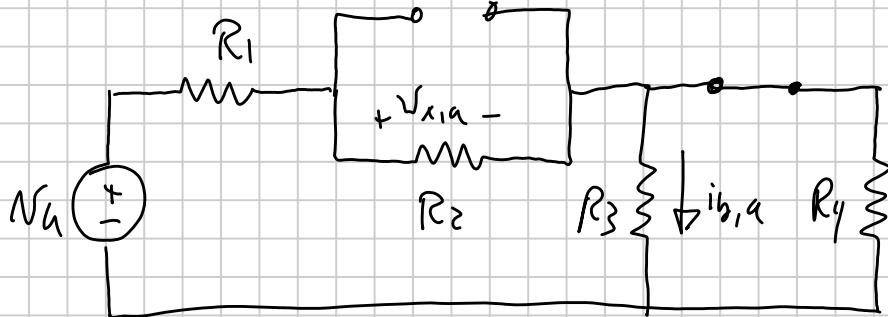


# ECE 110 Spring 14 Test B


Note Title

I)




$$V_{xa} = Na \frac{R_2}{R_1 + R_2 + (R_3 || R_y)} \text{ or } \frac{Na}{R_1 + R_2 + (R_3 || R_y)} R_2$$

$$i_{ya} = Na \frac{\frac{1}{R_1 + R_2 + (R_3 || R_y)}}{R_3 + R_y} \text{ or } Na \frac{R_3 || R_y}{R_1 + R_2 + (R_3 || R_y)} \frac{1}{R_3}$$

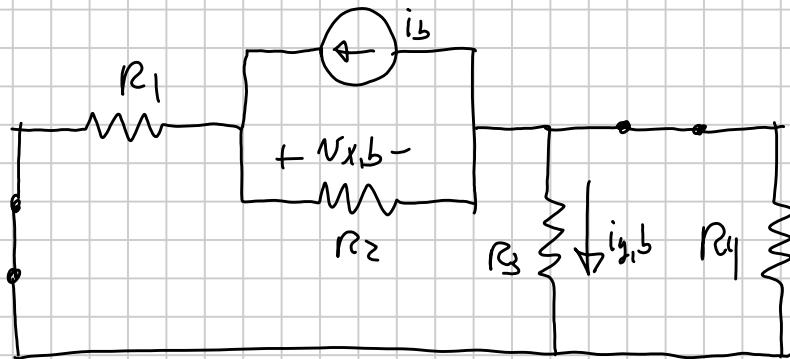

$$V_{xb} = i_b \left( R_2 || (R_1 + (R_3 || R_y)) \right) \text{ or } \frac{i_b (R_1 + (R_3 || R_y))}{R_2 + R_1 + (R_3 || R_y)} R_2$$

$$i_{yb} = -i_b \frac{R_2}{R_3 + (R_1 + (R_3 || R_y))} \frac{R_y}{R_3 + R_y}$$

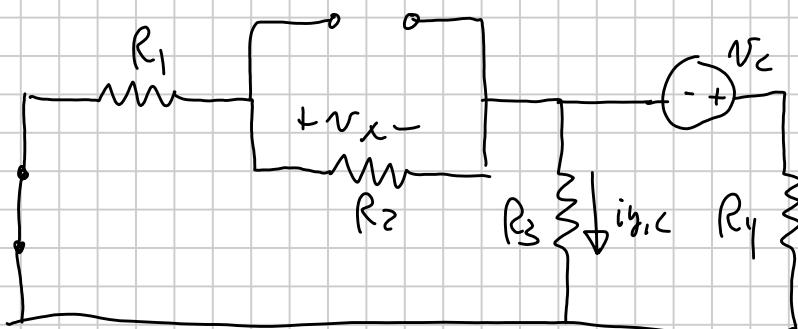

$$V_{xc} = V_c \frac{R_3 || (R_1 + R_2)}{R_4 + (R_3 || (R_1 + R_2))} \frac{R_2}{R_1 + R_2}$$

$$i_{yc} = -V_c \frac{R_3 || (R_1 + R_2)}{R_4 + (R_3 || (R_1 + R_2))} \frac{1}{R_3} \text{ or } \frac{-V_c}{R_4 + (R_3 || (R_1 + R_2))} \frac{R_1 + R_2}{R_1 + R_2 + R_3}$$

$$V_x = V_{x,a} + V_{x,b} + V_{x,c}$$

$$i_y = i_{y,a} + i_{y,b} + \underline{i_{y,c}}$$

(2)  $P_{dil}, V_a = V_a \left( \frac{V_1}{R_2} - i_b \right)$  (use KCL left of  $i_b$ )

$\text{or}$


$$V_a \left( \frac{V_a - (R_3 i_y + V_x)}{R_1} \right)$$

$$V_a \left( i_y + \frac{R_3 i_y + V_c}{R_4} \right) \quad (\text{KCL, GND})$$

$$P_{dil}, i_b = V_x i_b$$

$$P_{dil}, V_c = V_c \left( \frac{V_x}{R_2} - i_b - i_y \right) \text{ or}$$
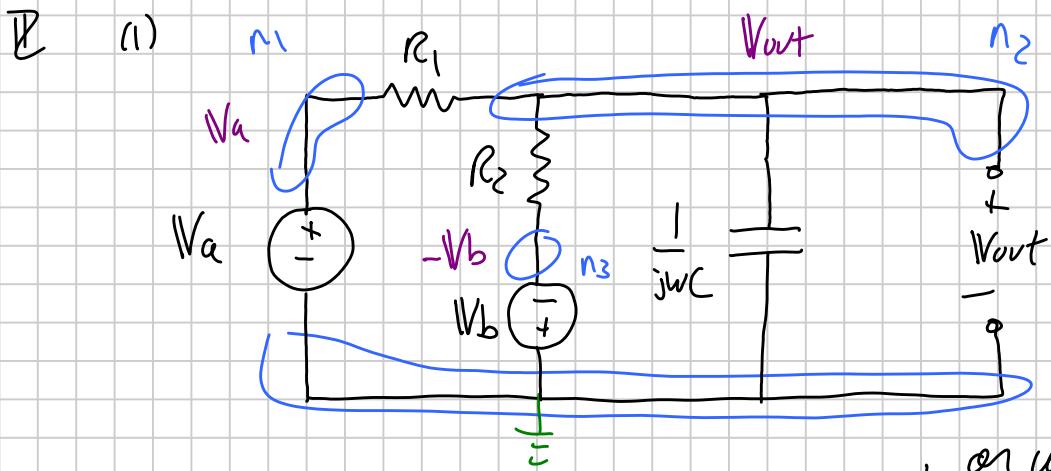
$$V_c \left( \frac{(R_3 i_y + V_c)}{R_4} \right)$$



$$KCL, n_2: \frac{V_{out} - V_a}{R_1} + \frac{V_{out} + V_b}{R_2} + \frac{V_{out}}{\frac{1}{jwC}} = 0$$

$$V_{out} \left( \frac{1}{R_1} + \frac{1}{R_2} + jwC \right) = \frac{V_a}{R_1} - \frac{V_b}{R_2}$$

$$V_{out} \left( \frac{jwC(R_1R_2 + R_1 + R_2)}{R_1R_2} \right) = \frac{V_aR_2 - V_bR_1}{R_1R_2}$$

$$V_{out} = \frac{V_aR_2 - V_bR_1}{jwCR_1R_2 + R_1 + R_2}$$

$$= \frac{6000V_a - 3000V_b}{jw(7200) + 9000}$$

or use superposition

$$\begin{aligned} V_{out,a} &= \frac{\frac{1}{jwC||R_2}}{\frac{1}{jwC||R_2} + R_1} V_a \\ &= \frac{R_2}{1 + jwCR_2} V_a \\ V_{out,b} &= -\frac{\frac{1}{jwC||R_1}}{\frac{1}{jwC||R_1} + R_2} V_b \\ V_{out,b} &= \frac{-R_1 V_b}{R_1 + R_2 + jwCR_1R_2} \end{aligned}$$

$\omega$	$V_a$	$V_b$	$V_{out}$
0	9	0	6

$$\rightarrow 1 \quad 4 \angle -108^\circ \quad 7 \angle 124^\circ \quad 3.51 \angle -122.5^\circ$$

$$3 \quad 0 \quad 5 \angle 160^\circ \quad 0.641 \angle -87.4^\circ$$


$$V_{out}(t) = 6 + 3.51 \cos(t - 122.5^\circ) + 0.641 \cos(3t - 87.4^\circ) \text{ V}$$

or do in two parts to get


$$V_{out,a, \omega=1} = 2.08 \angle -146.7^\circ$$

$$V_{out,b, \omega=1} = 1.82 \angle -94.7^\circ$$
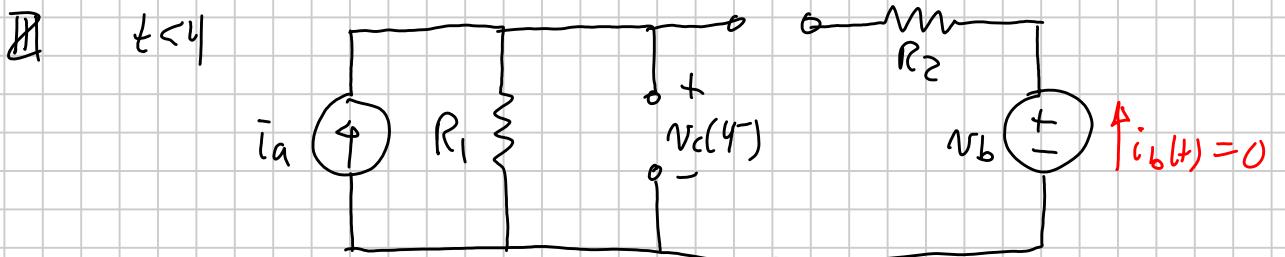
$$V_{out, \omega=1} = 3.51 \angle -122.5^\circ$$



$$V_c(4^-) = R_1 i_a = 1.05 V$$

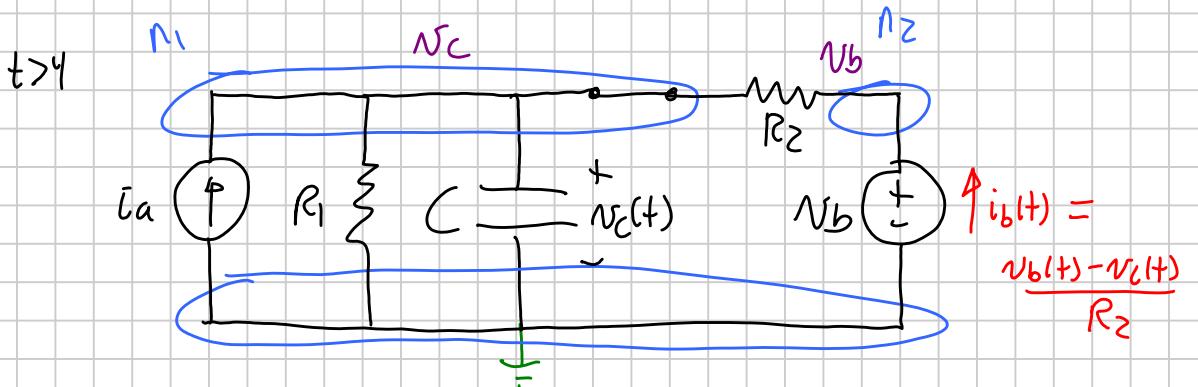

$$KCL_{n_1}: -i_a + \frac{V_c}{R_1} + C \frac{dV_c}{dt} + \frac{(V_c - V_b)}{R_2} = 0$$


$$C \frac{dV_c}{dt} + \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_c = i_a + \frac{V_b}{R_2}$$

$$\frac{C R_1 R_2}{R_1 + R_2} \frac{dV_c}{dt} + V_c = \frac{i_a R_1 R_2}{R_1 + R_2} + \frac{V_b R_1}{R_1 + R_2}$$

$$2.4 \frac{dV_c}{dt} + V_c = -0.873$$

$$V_c(t) = -0.873 + (1.05 - (-0.873)) e^{-(t-4)/2.4}$$
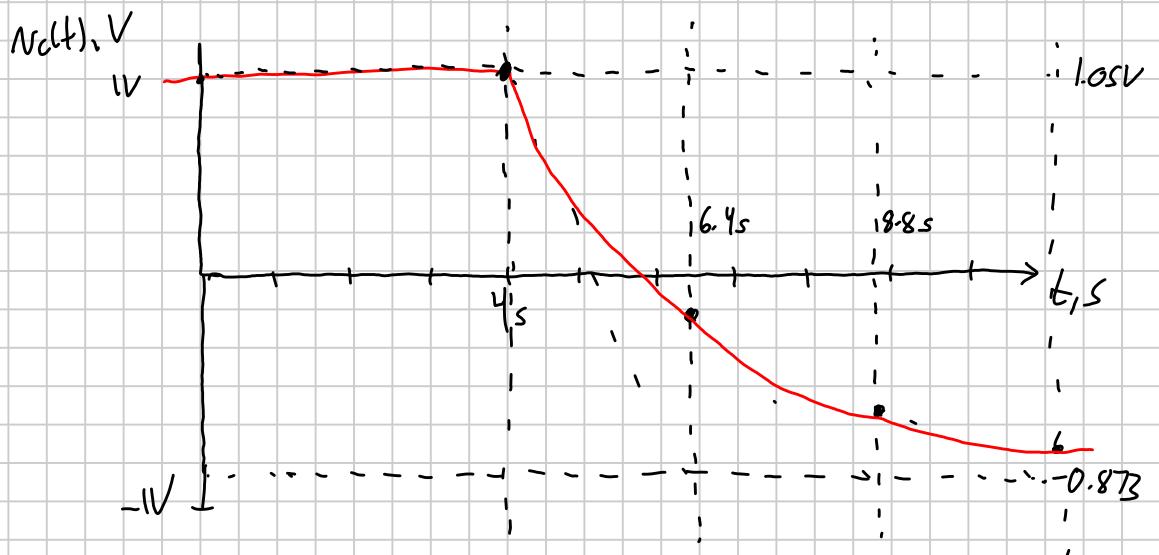
$$V_c(t) = -0.873 + 1.923 e^{-(t-4)/2.4} V \quad t > 4$$



$$(2) P_{\text{dell}, i_a}(t) = V_c(t) i_a = \begin{cases} 73.5 \text{ mW} & t < 4 \\ -61.1 + 134.6 e^{-(t-4)/2.4} \text{ mW} & t > 4 \end{cases}$$

$$(3) P_{\text{dell}, v_b}(t) = V_b i_b(t)$$

where  $V_b = -6$  and  $i_b(t) = \begin{cases} 0 & \text{switch open!} \\ 0 & t < 4 \\ \frac{V_b - V_c(t)}{R_2} = \frac{-5.127 - 1.923}{40000} e^{-(t-4)/2.4} & t > 4 \end{cases}$

so,  $P_{\text{dell}, v_b}(t) = \begin{cases} 0 & W \\ 0.169 + 0.288 e^{-(t-4)/2.4} \text{ mW} & t > 4 \end{cases}$

$$\text{TP} \quad (1) \quad \omega_0 = 200 \text{ rad/s} \quad T = \frac{2\pi}{\omega_0} = 0.01\pi = 0.0314 \text{ s.}$$

$$N_{0,\text{in}} = 3$$

$$V_{4,\text{in}} = 1L9^{\circ}$$

$$V_{9,\text{in}} = 7L - 156^{\circ}$$

$$V_{11,\text{in}} = 15L - 79^{\circ}$$


$$(2) \quad (\text{a}) \quad \text{HPF}; \quad \lim_{\omega \rightarrow 0} |H(j\omega)| = 0 \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = 1$$

max gain = 1       $\omega_{HP} = 1100$

(b)

$n$	$n\omega_0$	$V_{n,\text{in}}$	$H(jn\omega_0)$	$V_{n,\text{out}}$
0	0	3	0	0 $\leftarrow N_{0,\text{out}}$
4	800	1L9 <sup>°</sup>	0.588L53.97 <sup>°</sup>	0.588L62.97 <sup>°</sup>
9	1800	7L-156 <sup>°</sup>	0.853L31.43 <sup>°</sup>	5.97L-124.6 <sup>°</sup>
11	2200	15L-79 <sup>°</sup>	0.891L26.57 <sup>°</sup>	13.4L-52.43 <sup>°</sup>

(c) HPF

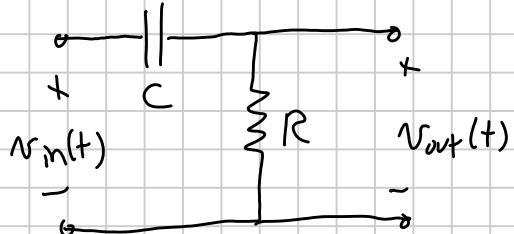

$$H = \frac{R}{j\omega C + R} = \frac{j\omega CR}{j\omega CR + 1} = \frac{j\omega}{j\omega + \frac{1}{CR}}$$

$$\frac{1}{CR} = 1100$$

$$C = \frac{1}{1100R} = 6.06 \times 10^{-8}$$

$$= 60.6 \text{ nF}$$

$$(d) \quad V_{\text{out}}(t) = 0.588 \cos(800t + 62.97^{\circ}) + 5.97 \cos(1800t - 124.6^{\circ}) + 13.4 \cos(2200t - 52.43^{\circ}) \quad \boxed{V}$$

(e) only keep terms  $\omega > \omega_0$  at 1100, so

$$v_x(t) = 7 \cos(1800t - 156^{\circ}) + 15 \cos(2200t - 79^{\circ}) \quad \boxed{V}$$

(ok if written as original)