

Duke University
Edmund T. Pratt, Jr. School of Engineering

EE 61L Section 2, Fall 2001

Test II

Michael R. Gustafson II


Name (please print)_____

In keeping with the Honor Code, I have neither provided nor received any assistance on this test. I understand if it is later determined that I gave or received assistance, I will fail the class and will be brought before the Undergraduate Judicial Board.

Signature:_____

Problem I: [25 pts.] Superposition

Given the following circuit:

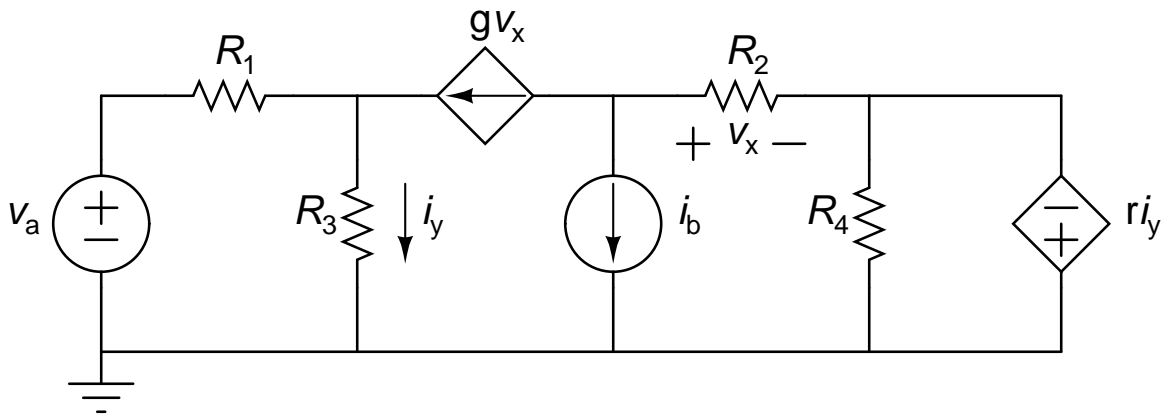


and known values r , g , R_1 , R_2 , R_3 , R_4 , v_a , and i_b , find p_{abs, R_4} using superposition. You *must* redraw the circuit each time to get full credit for this problem.

Name (please print):

Honor Code (please initial):

Problem II: [20 pts.] Thévenin-Norton

Given the following circuit:

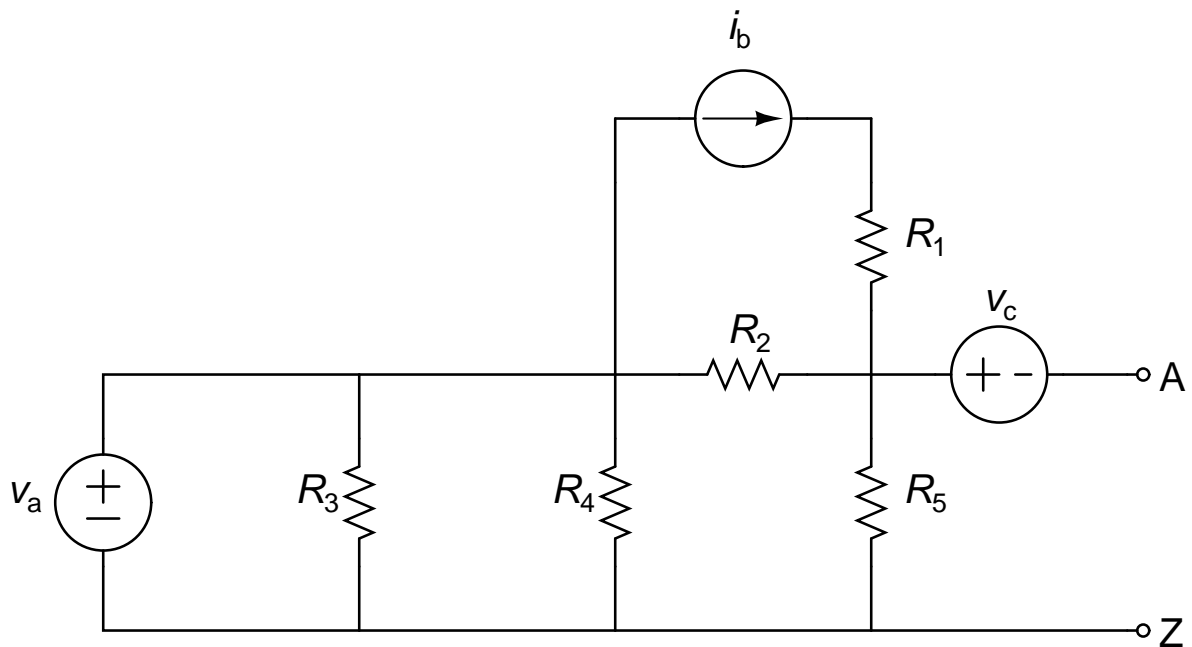


and known values R_1 , R_2 , R_3 , R_4 , R_5 , v_a , i_b , and v_c , determine *and draw* both the Thévenin and Norton equivalent circuits as seen at terminals A-Z.

Name (please print):

Honor Code (please initial):

Problem III: [25 pts.] Operational Amplifiers

Given the following circuit:

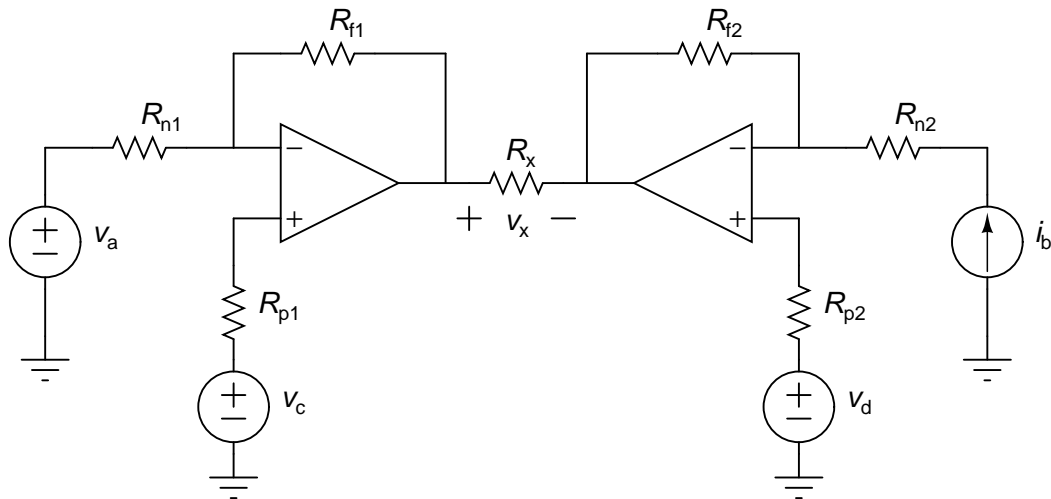


and known values R_{n1} , R_{f1} , R_{p1} , R_{n2} , R_{f2} , R_{p2} , R_x , v_a , i_b , v_c , and v_d , find v_x in terms of the known values. You may assume both operational amplifiers are ideal.

Name (please print):

Honor Code (please initial):

Problem IV: [30 pts.] Inductors and Capacitors

Given the following circuit:

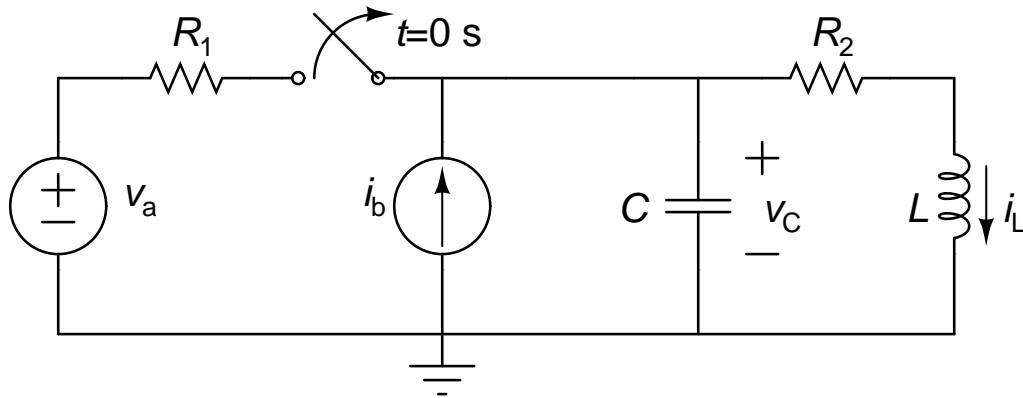

and known values R_1 , R_2 , L , C , v_a , and i_b ,

- (1) Assume that the two independent sources are constant and that this circuit has been in place for a very long time before $t = 0$ s. Determine the capacitor voltage v_C and inductor current i_L for time $t = 0^-$ s.
- (2) Determine the capacitor current i_C and inductor voltage v_L for time $t = 0^+$ s. You may assume that the values of the state variables $v_C(0^+)$ and $i_L(0^+)$ are known, but *not* that the *derivatives* of the state variables are known.
- (3) Assume that the two independent sources are constant and that this circuit has been in place for a very long time after $t = 0$ s. Determine the capacitor voltage v_C and inductor current i_L for time $t \rightarrow \infty$ s.
- (4) Find a differential equation for i_L in terms of the known values for $t > 0$ s. If done correctly, you will end up with a *second* order differential equation. *Hint:* use v_C and i_L as your only unknowns to develop two equations for the circuit, then substitute one into the other to get a single equation with i_L and its derivatives.