

Duke University  
Edmund T. Pratt, Jr. School of Engineering

EE 61 Section 2, Spring 2001

**Test I**

Michael R. Gustafson II

---

Name (please print)\_\_\_\_\_

In keeping with the Honor Code, I have neither provided nor received any assistance on this test. I understand if it is later determined that I gave or received assistance, I will fail the class and will be brought before the Undergraduate Judicial Board.

Signature:\_\_\_\_\_

---


**Problem I: [15 pts] Element Table**

Fill in the table below. For the **Equation** column, you can put *any* equation for the given variable in terms of other variables.

Name	Variable	Units	Equation
charge			(blank)
current			
work			(blank)
voltage			
power			
resistance			
conductance			(blank)

## Problem II: [15 pts] Basic Circuit Relationships

Given the following circuit:

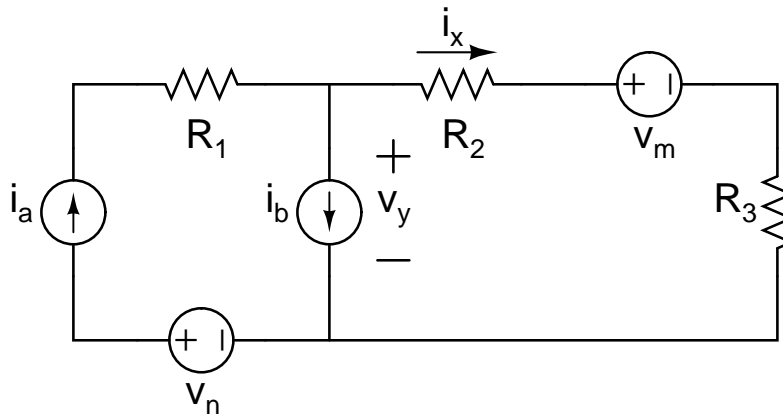

and known values  $i_a$ ,  $i_b$ ,  $v_m$ ,  $v_n$ ,  $R_1$ ,  $R_2$ , and  $R_3$ , find the following quantities in terms of the known values:

(1)  $i_x$

(2)  $v_y$

(3)  $p_{\text{abs}, v_n}$


(4)  $p_{\text{del}, R_1}$

(5)  $p_{\text{abs}, R_3}$

(6)  $p_{\text{del}, i_b}$

### Problem III: [30 pts] Node Voltage Method


Given the following circuit:

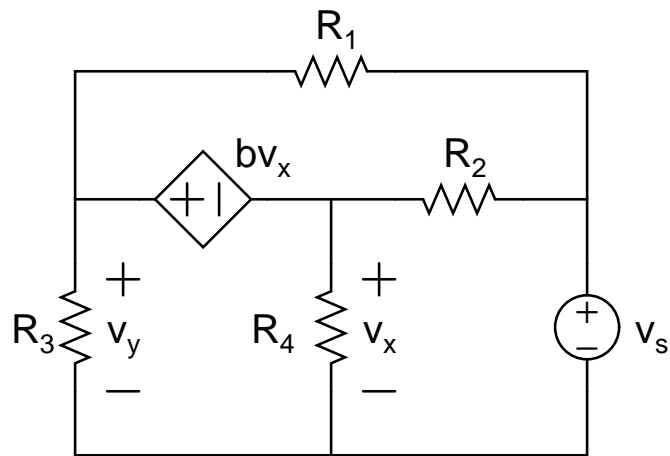

and known values  $v_s$ ,  $b$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ , find  $v_y$  in terms of the known values using the Node Voltage Method.

#### Problem IV: [30 pts] Mesh Current Method

Given the following circuit:

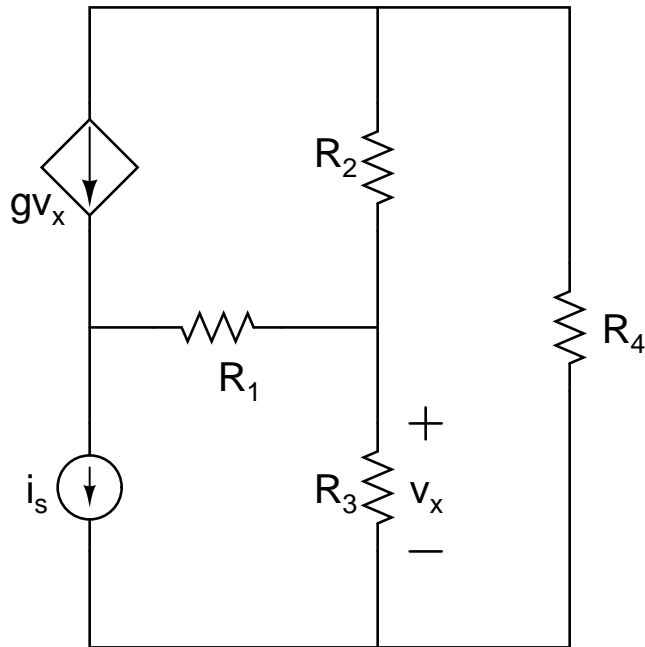

and known values  $i_s$ ,  $g$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ , find  $p_{\text{abs}, R_4}$  in terms of the known values using the Mesh Current Method. *Hint: use the two simple-source equations first to get a single equation for the unknown current in the tallest mesh.*

**Problem V: [10 pts] Cramer's Rule**

Given the following set of three linear equations:

$$x + 5y - 7z = 10$$

$$-8x - 2y + 3z = 11$$

$$6x + 9y - 4z = 12$$

(1) Write the system as a matrix equation

(2) Set up, but do not solve, what you would need to do to find the value of the variable  $y$