

Duke University
Edmund T. Pratt, Jr. School of Engineering

EE 61 Section 2, Spring 2001

Test IV

Michael R. Gustafson II


Name (please print)_____

In keeping with the Honor Code, I have neither provided nor received any assistance on this test. I understand if it is later determined that I gave or received assistance, I will fail the class and will be brought before the Undergraduate Judicial Board.

Signature:_____


Problem I: [30 pts] Thévenin-Norton Equivalent Circuits

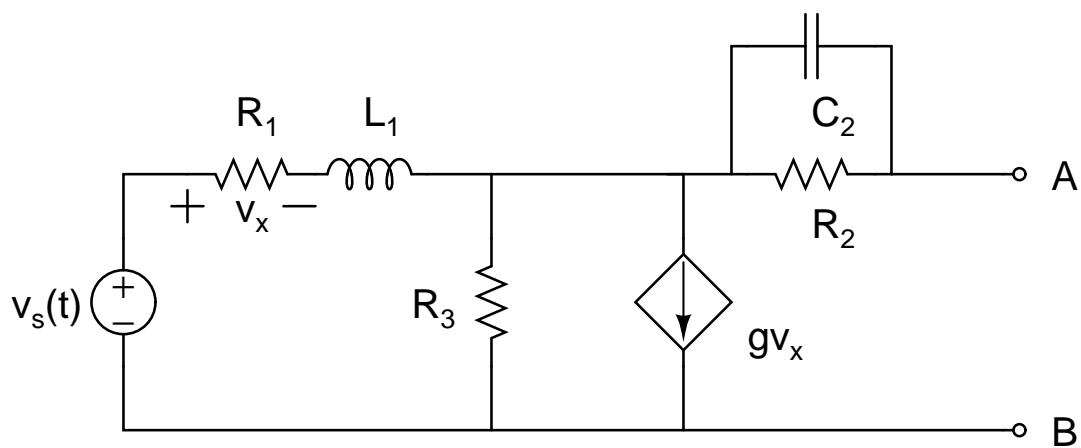- (1) Assuming you have a circuit where $V_{oc} = 8\angle 7^\circ$ V, $I_{sc} = 4\angle 23^\circ$ A, and $\omega = 10$ rad/s, draw two Norton equivalent circuits - one with the passive elements in series and one with them in parallel.



- (2) Given the circuit above and the known values $v_s(t)$, C_2 , L_1 , R_1 , R_2 , R_3 , and g , find V_{oc} , I_{sc} , and Z_{th} as seen across terminals A-B.

Problem II: [30 pts] Complex Power

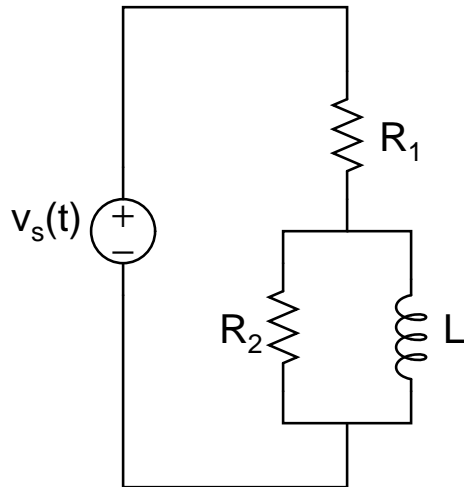

Given the circuit above and the known values:


$$v_s(t) = 5 \cos(377t + 8^\circ) \text{ V}$$

$$L = 650 \text{ mH}$$

$$R_1 = 300 \, \Omega$$

$$R_2 = 700 \, \Omega$$

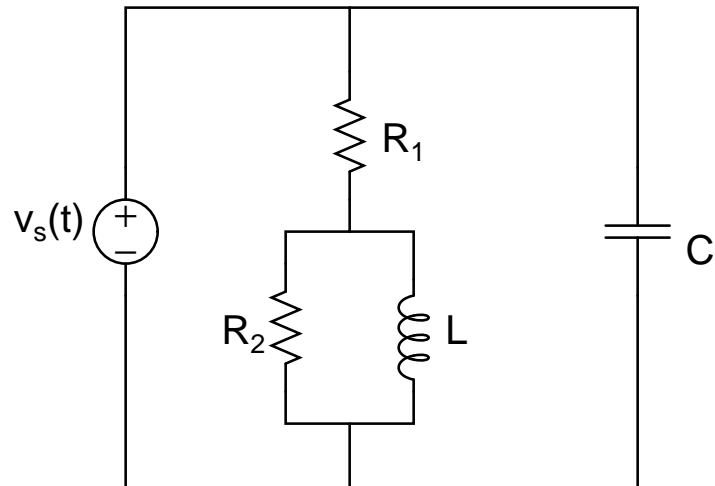
- (1) Find the equivalent impedance \mathbb{Z} as seen by the voltage source
- (2) Find the complex power delivered by the voltage source, \mathbb{S}_{del}
- (3) Find the power factor; be sure to indicate if it is **lagging** or leading (hint hint)



Assume you add a $5\ \mu\text{F}$ capacitor in parallel with the voltage source as shown above.

- (a) Find the equivalent impedance \mathbb{Z} as seen by the voltage source
- (b) Find the complex power delivered by the voltage source, \mathbb{S}_{del}
- (c) Find the power factor; be sure to indicate if it is lagging or leading


Problem III: [20 pts] Transformers

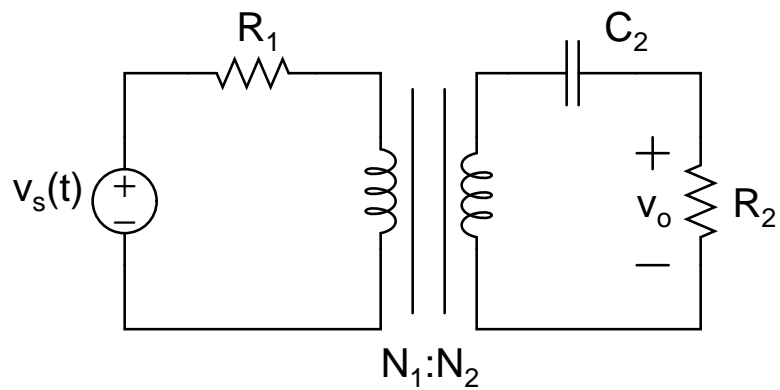

Given the circuit above and known values $v_s(t)$, C_2 , R_1 , R_2 , N_1 , and N_2 , find the network function:

$$\mathbb{H}(j\omega) = \frac{\mathbb{V}_o}{\mathbb{V}_s}$$

Problem IV: [20 pts] Mutual Inductance

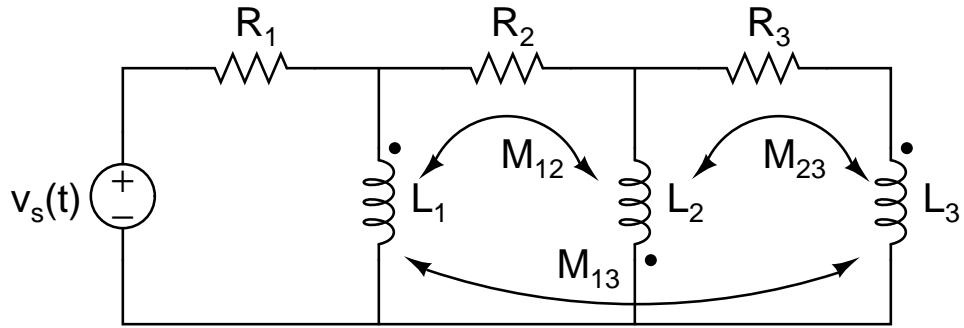

Given the circuit above and known values $v_s(t)$, L_1 , L_2 , L_3 , M_{12} , M_{13} , M_{23} , R_1 , R_2 , R_3 , write the three mesh current equations in the frequency domain *or* in the time domain.