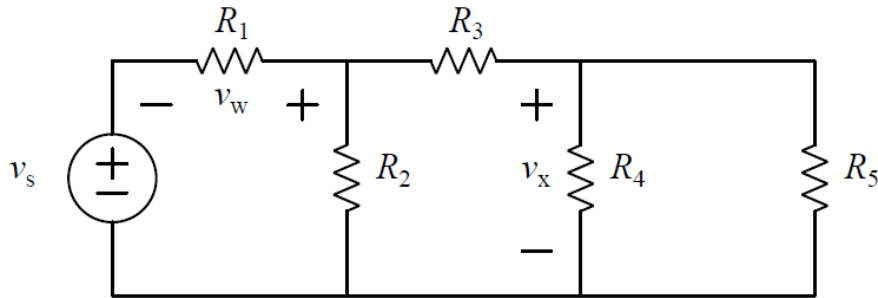


1

Tuesday, March 2, 2021


(1)



$$R_{45} = R_4 \parallel R_5 \quad R_{345} = R_3 + R_{45} \quad R_{2345} = R_2 \parallel R_{345}$$

$$v_w = \frac{-v_s R_1}{R_1 + R_{2345}} \quad v_x = \frac{v_s R_{2345}}{R_1 + R_{2345}} \quad \frac{R_4 \parallel R_5}{R_3 + R_4 \parallel R_5}$$

(2)

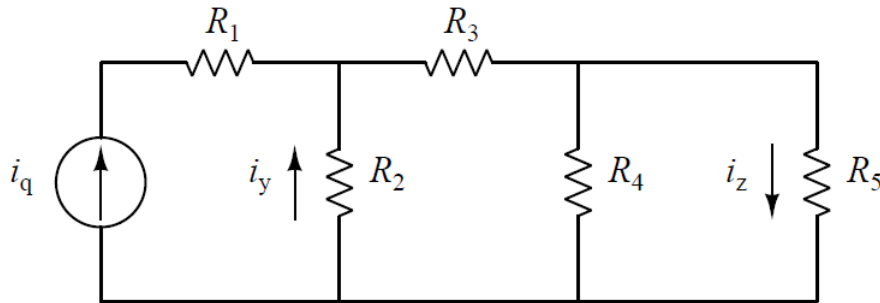


$$R_{45} = R_4 \parallel R_5 \quad R_{345} = R_3 + R_{45} \quad R_{2345} = R_2 \parallel R_{345}$$

NOTE: R<sub>1</sub> NOT INVOLVED IN DIVISION!

$$i_y = \frac{-i_q (R_2 \parallel R_{345})}{R_2} \quad i_z = \frac{i_q (R_2 \parallel R_{345})}{R_{345}} \quad \frac{R_4 \parallel R_5}{R_5}$$
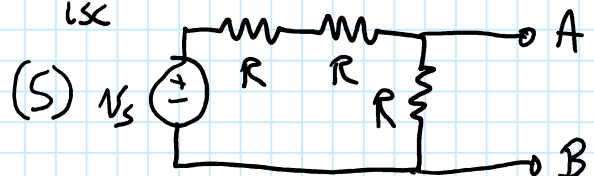
$$(3) \quad v_{oc} = 0.5 \text{ V} \quad i_{sc} = 375 \mu\text{A}, \quad R_{Th} = \frac{v_{oc}}{i_{sc}} = 1333.3 \Omega$$




$$(4) \quad R_L = R_{Th} = 1333.3 \Omega$$

$$P_{del} = \frac{v_{oc}^2}{4R_L} = 46.88 \mu\text{W}$$

$$R_{eq} = R \parallel 2R = \frac{2R}{3} \checkmark$$
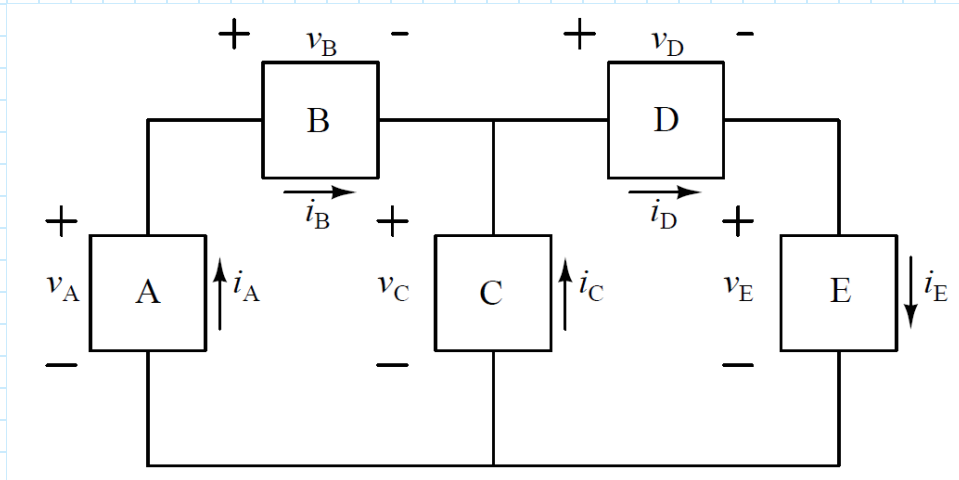
$$v_{oc} = \frac{v_s R}{\frac{2R}{3}} \checkmark$$




Element	Conv.	Voltage $v$ , V	Current $i$ , A	Power Absorbed $p_{\text{abs}}$ , W
A	A	15	$i_A = i_B = 3$	$p = -vi = -45$
B	P	$-v_A + v_B + v_C = 0$ 5	3	$p = vi = 15$
C	A	$v = -p/i = 10$	$i_C = i_D - i_B = -1$	10
D	P	$-v_C + v_D + v_E = 0$ 12	2	$p = vi = 24$
E	P	-2	$i_E = i_D = 2$	$p = vi = -4$

$$\text{CHECK: } \sum p_{\text{abs}} = -45 + 15 + 10 + 24 - 4 = 0 \checkmark$$

$$\text{KVL, left: } -v_A + v_B + v_C = -15 + 5 + 10 = 0 \checkmark$$

$$\text{KVL, right: } -v_C + v_D + v_E = -10 + 12 - 2 = 0 \checkmark$$
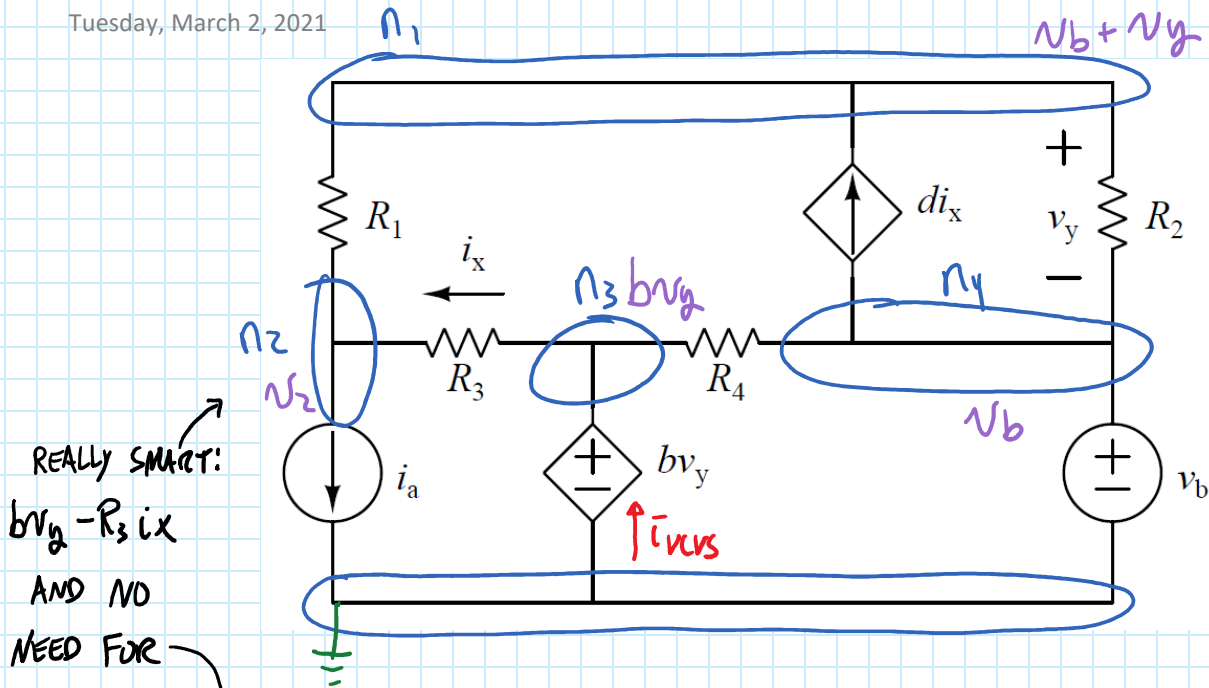
$$\text{KCL, top middle: } -i_B - i_C + i_D = -3 + 1 + 2 = 0 \checkmark$$



$$\# KCL = \text{nodes} - 1 - \text{v. src} = 5 - 1 - 2 = 2$$

$$\text{UNK: } v_2, v_y, i_x \quad (\text{LAZY LABELS MAY ADD } v_1, v_3, v_4)$$

$$KCL, n_1: \frac{v_b + v_y - v_2}{R_1} - di_x + \frac{v_y}{R_2} = 0$$

$$KCL, n_2: \frac{v_2 - (v_b + v_y)}{R_1} - i_x + i_a = 0$$

$$\text{MEAS, } i_x: i_x = \frac{b v_y - v_2}{R_3}$$

IF LAZY LABELS,  
 SRC, v\_b:  $v_b = v_4 - 0$   
 SRC, vcs:  $b v_y = v_3 - 0$   
 MEAS, v\_y:  $v_y = v_1 - v_4$

$$P_{\text{abs}, R_1} = (b v_y - v_b)^2 / R_1$$

$$P_{\text{del}, \text{ccs}} = di_x v_y$$


$$P_{\text{del}, \text{vcs}} = i_{\text{vcs}} \cdot b v_y$$

$$KCL, n_3: i_x + \frac{(b v_y - v_b)}{R_1} - i_{\text{vcs}} = 0$$

$$i_{\text{vcs}} = i_x + \frac{(b v_y - v_b)}{R_1}$$

# 4 -MCM

Tuesday, March 2, 2021

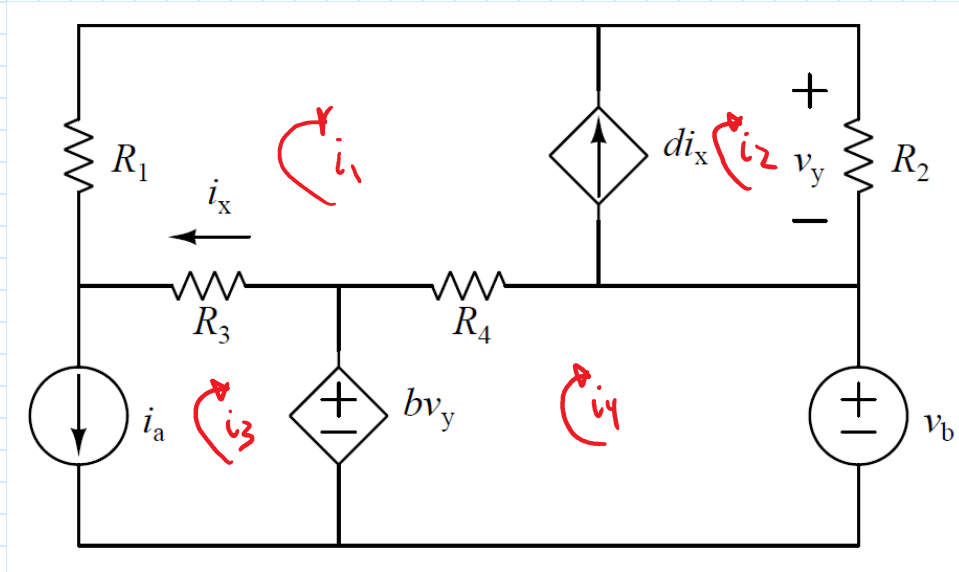

$$\# KVL = \text{mesh} - i. \text{src} = 4 - 2 = 2$$

$$\text{UNK: } i_1 \ i_2 \ i_3 \ i_4 \ i_x \ v_y$$

$$KVL, sl_{12}: R_1 i_1 + R_2 i_2 + R_4 (i_1 - i_4) + R_3 (i_1 - i_3) = 0$$

$$KVL, l_4: -bv_y + R_4 (i_4 - i_1) + v_b = 0$$

$$SRC, i_a: i_a = -i_3$$

$$SRC, di_x: di_x = i_2 - i_1$$

$$MEAS, i_x: i_x = i_1 - i_3$$

$$MEAS, v_y: v_y = R_2 i_2$$


$$p_{abs, R_4} = (i_1 - i_4)^2 R_4$$

$$p_{del, cc_s} = di_x v_y$$

$$p_{del, vcv_s} = bv_y (i_4 - i_3)$$

# 4 - BCM

Tuesday, March 2, 2021

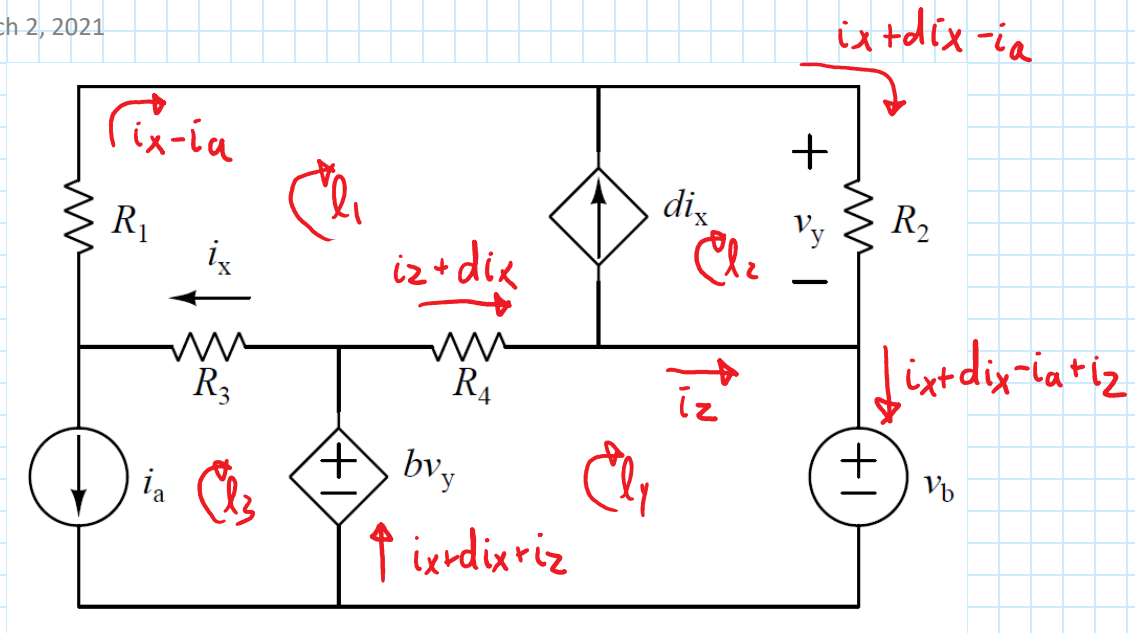

UNK:  $i_x, i_z, v_y$


$$\begin{cases} \text{KVL, } l_2: R_1(i_x - i_a) + R_2(i_x + d i_x - i_a) - R_4(i_z + d i_x) + R_3 i_x = 0 \\ \text{KVL, } l_4: -b v_y + R_4(i_z + d i_x) + v_b = 0 \\ \text{MEAS, } v_y: v_y = R_2(i_x + d i_x - i_a) \end{cases}$$

$$P_{\text{abs}, R_4} = (i_z + d i_x)^2 R_4$$

$$P_{\text{dd}, \text{CCCS}} = d i_x v_y$$

$$P_{\text{dd}, \text{VCVS}} = (i_x + d i_x + i_z) b v_y$$


Tuesday, March 2, 2021

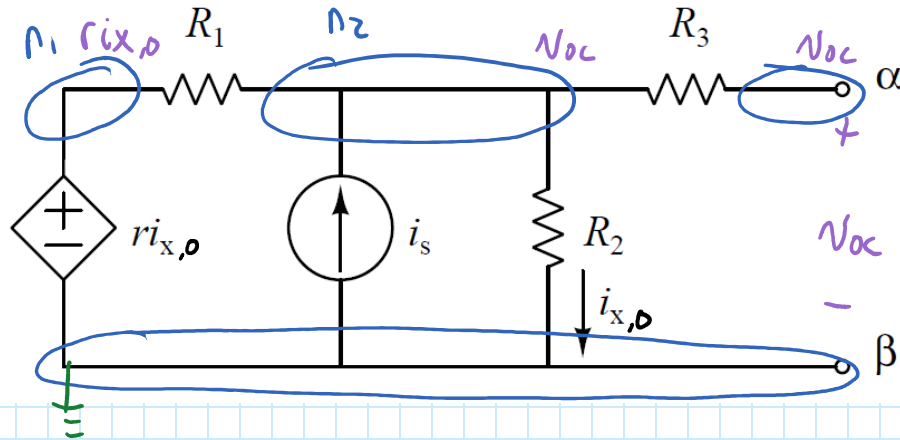INDEP + DEP → FIND  $N_{oc}, i_{sc}, R_{Th} = V_{oc}/i_{sc}$ OHM'S LAW ON  $R_2$ :  $R_2 i_{x,o} = V_{oc}$ KCL,  $n_2$ :  $\frac{V_{oc} - r i_{x,o}}{R_1} - i_s + i_{x,o} = 0$  (SUBS  $\rightarrow$  &  $\times R_1$ )

$$R_2 i_{x,o} - r i_{x,o} - R_1 i_s + R_2 i_{x,o} = 0$$

$$i_{x,o} = \frac{R_1 i_s}{R_1 + R_2 - r}$$
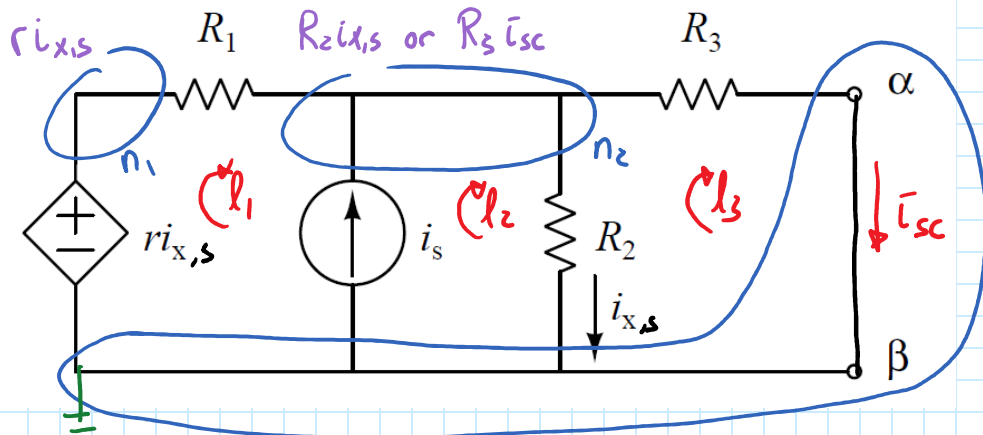
$$V_{oc} = \frac{R_1 R_2 i_s}{R_1 + R_2 - r}$$



$$KV, l_3: -R_2 i_{x,s} + R_3 i_{sc} = 0 \quad i_{sc} = \frac{R_2 i_{x,s}}{R_3}$$

$$KCL, n_2: \frac{R_2 i_{x,s} - r i_{x,s}}{R_1} - i_s + i_{x,s} + \frac{R_2 i_{x,s}}{R_3} = 0$$

# 5 - continued



Tuesday, March 2, 2021

$$i_{x,s} = \frac{\bar{i}_s}{\frac{R_2 - r}{R_1} + 1 + \frac{R_2}{R_3}} = \frac{R_1 R_3 \bar{i}_s}{R_2 R_3 - r R_3 + R_1 R_3 + R_1 R_2} \quad i_{sc} = \frac{R_2 i_{x,s}}{R_3} = \frac{R_1 R_2 \bar{i}_s}{R_1 R_2 + R_1 R_3 + R_2 R_3 - r R_3}$$

$$V_{oc} = \frac{R_1 R_2 \bar{i}_s}{R_1 + R_2 - r}$$

$$i_{sc} = \frac{R_1 R_2 \bar{i}_s}{R_1 R_2 + R_1 R_3 + R_2 R_3 - r R_3}$$

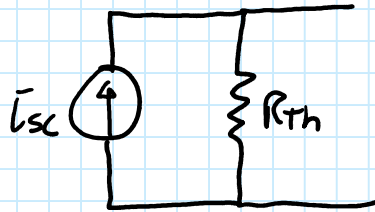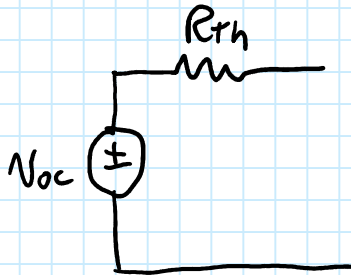
$$R_{Th} = \frac{V_{oc}}{i_{sc}} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3 - r R_3}{R_1 + R_2 - r} = R_3 + \frac{R_1 R_2}{R_1 + R_2 - r}$$



$$R_L = R_{Th}$$

$$P_{del} = \frac{V_{oc}^2}{4 R_{Th}} = \frac{i_{sc}^2 R_{Th}}{4}$$

check: if  $r = 0$ ,

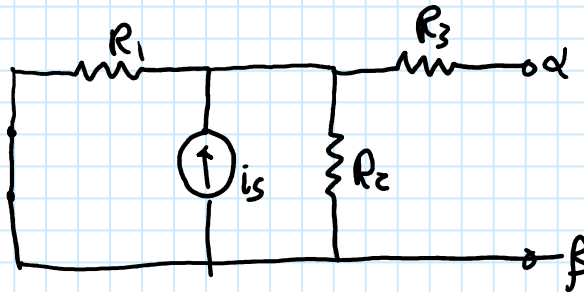

$$V_{oc} = \frac{R_1 R_2 \bar{i}_s}{R_1 + R_2} = (R_1 \parallel R_2) \bar{i}_s \quad \checkmark$$

$$i_{sc} = \frac{R_1 R_2 \bar{i}_s}{R_1 R_2 + R_1 R_3 + R_2 R_3} = \frac{(R_1 \parallel R_2 \parallel R_3) \bar{i}_s}{R_3} \quad \checkmark$$

$$R_{Th} = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1 + R_2} = R_3 + \frac{R_1 R_2}{R_1 + R_2} = R_3 + (R_1 \parallel R_2) \quad \checkmark$$