

Problem 1

Tuesday, April 6, 2021

(1) $80 + 40 = 120 \text{ mH}$

$$120 \text{ mH} \parallel 20 \text{ mH} = \frac{120 \cdot 20}{120 + 20} = 17.14 \text{ mH}$$


$$17.14 \text{ mH} + 10 \text{ mH} = 27.14 \text{ mH}$$

(2) $\frac{40 \cdot 80}{40 + 80} = 26.67 \mu\text{F}$

$$26.67 + 20 = 46.67 \mu\text{F}$$

$$\frac{46.67 \cdot 10}{46.67 + 10} = 8.235 \mu\text{F}$$


(3) ① 2000 rad/s:

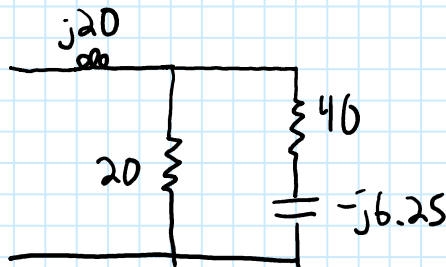

$$(40 - j6.25) \parallel 20 = 13.42 \angle -2.934^\circ$$

$$13.42 \angle -2.934^\circ + j20 = 23.51 \angle 55.21^\circ \Omega = 13.41 + j19.31 \Omega$$

(4) DCSS:

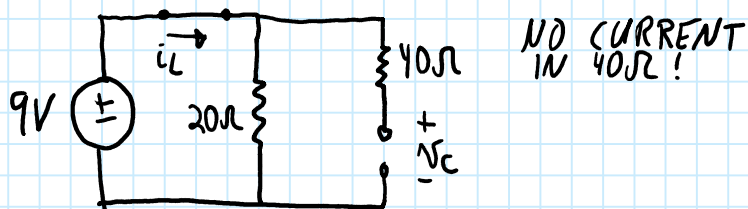


$$i_L = \frac{9}{20} = 0.45 \text{ A} \quad E = \frac{1}{2} L i^2 = 1.0125 \text{ mJ}$$


$$v_c = 9 \text{ V} \quad E = \frac{1}{2} C v^2 = 3.240 \text{ mJ}$$

$E_R = 0$ ALWAYS!

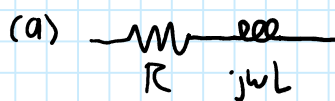(5) $Z = 700 + j100 \Omega$ $X > 0$ MEANS INDUCTOR


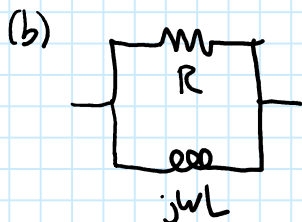
$$R = 700 \Omega \quad \omega L = 100 \Rightarrow L = \frac{100}{5000} = 20 \text{ mH}$$



$$Y = \frac{1}{Z} = 1.4 - 0.2j \text{ mS} = \frac{1}{R} + \frac{1}{j\omega L}$$


$$R = \frac{1}{1.4 \cdot 10^{-3}} = 714.3 \Omega$$

$$L = \frac{1}{0.2 \cdot 10^{-3} \cdot 5000} = 1 \text{ H}$$

Problem 2

Tuesday, April 6, 2021

(1) DCSS:

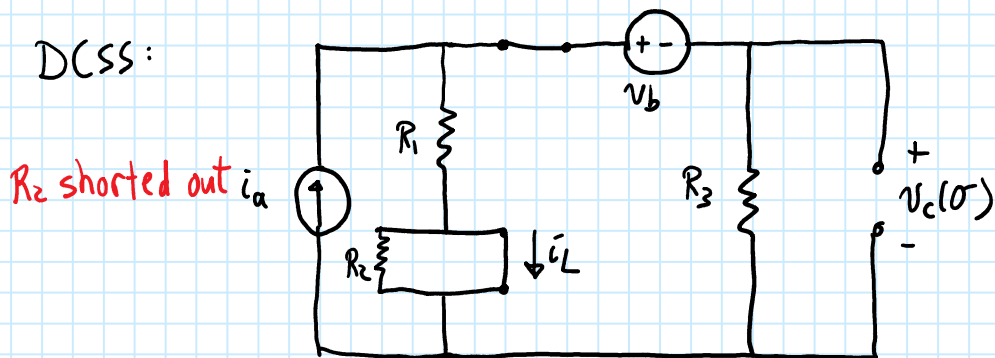


$$V_c(0^-) = i_a(R_1 \parallel R_3) - \frac{V_b R_3}{R_1 + R_3} = \frac{i_a R_1 R_3 - V_b R_3}{R_1 + R_3}$$

$$i_c(0^-) = 0 \quad \text{AND} \quad V_L(0^-) = 0$$

$$i_L(0^-) = \frac{i_a(R_1 \parallel R_3)}{R_1} + \frac{V_b}{R_1 + R_3} = \frac{i_a R_3 + V_b}{R_1 + R_3}$$

$t = 0^+$

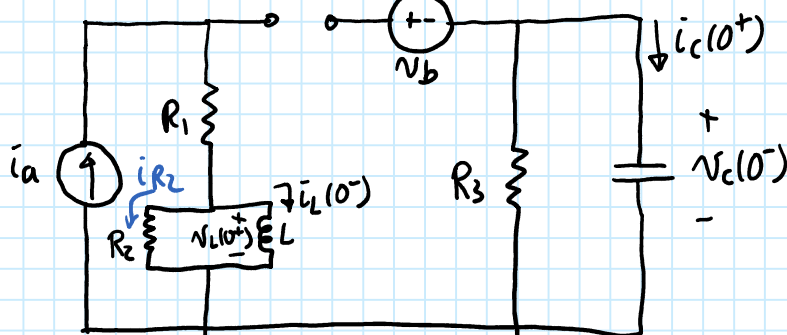


$$V_c(0^+) = V_c(0^-) \quad \text{AND} \quad i_L(0^+) = i_L(0^-)$$

$$V_L(0^+) = R_2(i_a - i_L(0^-)) \quad \text{BCM} \quad i_{R_2} = i_a - i_L(0^-)$$

$$V_c(0^+) = -R_3 i_c(0^+)$$

(2) $i_L(0^-) = \frac{i_a(R_1 \parallel R_3)}{R_1} + \frac{V_b}{R_1 + R_3} = (4 - 2) = 2 \text{ mA}$

$t > 0$:

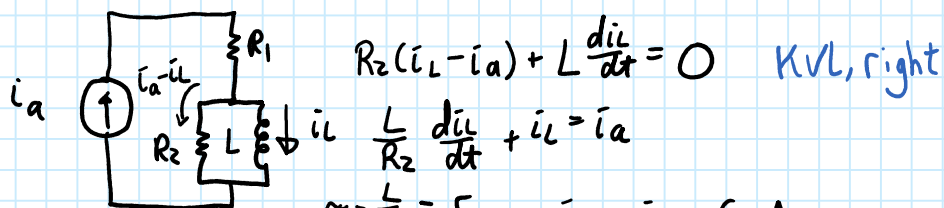


$$R_2(i_L - i_a) + L \frac{di_L}{dt} = 0 \quad \text{KVL, right}$$

$$\frac{L}{R_2} \frac{di_L}{dt} + i_L = i_a$$

$$\tau = \frac{L}{R_2} = 5 \mu\text{s} \quad i_{L,\infty} = i_a = 6 \text{ mA}$$


$$i_L(t) = i(\infty) + (i(0) - i(\infty))e^{-t/\tau}$$

$$= (6 - 4)e^{-t/5 \cdot 10^{-6}} \text{ mA}$$

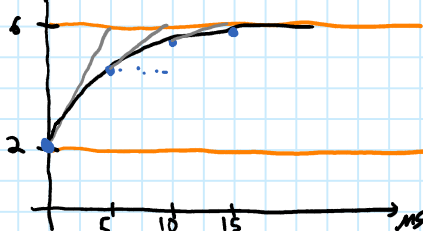

Problem 3

Tuesday, April 6, 2021

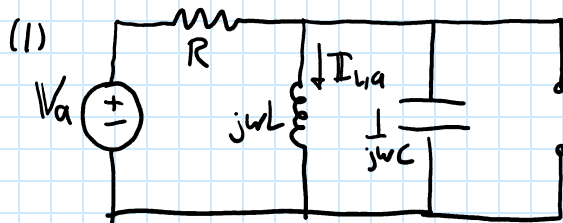


$$Z_{LC} = \frac{jwL}{\frac{jwL}{jwC} + 1} = \frac{jwL}{(jw)^2 LC + 1}$$

$$I_{L,a} = \frac{V_a}{R + Z_{LC}} \cdot \frac{1}{jwL} = \frac{V_a}{R + \frac{jwL}{(jw)^2 LC + 1}} \cdot \frac{1}{jwL}$$

$$= \frac{V_a}{(jw)^2 LRC + jwL + R}$$
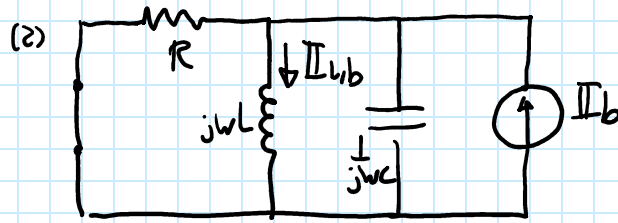
$$H_a = \frac{I_{L,a}}{V_a} = \frac{1}{(jw)^2 LRC + jwL + R}$$



$$Z_{LRC} = R \parallel jwL \parallel \frac{1}{jwC} = \frac{1}{\frac{1}{R} + \frac{1}{jwL} + jwC} = \frac{jwLR}{(jw)^2 LRC + jwL + R}$$

$$I_{L,b} = \frac{Z_{LRC}}{jwL} I_b = \frac{R I_b}{(jw)^2 LRC + jwL + R}$$

$$H_b = \frac{I_{L,b}}{I_b} = \frac{R}{(jw)^2 LRC + jwL + R}$$

ω	V_a	H_a	I_b	H_b	I_L
0	3	.001	.008	1	.011
8000	$6 \angle 19^\circ$	$4.166 \cdot 10^{-4} \angle -89.05^\circ$	0	X	$.002500 \angle -70.05^\circ$
20000	0	X	$.005 \angle -117^\circ$	$0.128 \angle -130^\circ$	$.0006402 \angle 113^\circ$

$$\bar{i}_L(t) = 11 + 2.5 \cos(8000t - 70.05^\circ) + 0.6402 \cos(20000t + 113^\circ) \text{ mA}$$

(4)/(5) LOOKS LIKE LOW; CHECK DAMPING

$$(jw)^2 LRC + jwL + R \rightarrow (jw)^2 + jw \frac{1}{RC} + \frac{1}{LC}$$

$$\omega_n = \sqrt{\frac{1}{LC}} = 8165 \quad 2\beta\omega_n = \frac{1}{RC} \quad \beta = \frac{1}{2\omega_n RC} = 1.225$$

OVERDAMPED \rightarrow LPF?

Problem 4

Tuesday, April 6, 2021

(1) $\frac{5j\omega}{j\omega + 20} = \frac{1}{4} \frac{j\omega}{(1 + j\frac{\omega}{20})}$

$20 \log_{10} |H|$

$|H| \approx \frac{1}{4} \cdot \left(\frac{20}{\omega}\right) = 5 \rightarrow 14 \text{ dB}$

20 dB/dec

$\omega = 20$

14 dB

90°


$-45^\circ/\text{dec}$

0°

(c) HPF, $|H| > \frac{|H|_{\max}}{\sqrt{2}}$ $\omega \geq 20$, $\text{MAX GAIN} = 5 \text{ or } 14 \text{ dB}$

(d) $(j\omega + 20)V_{\text{out}} = 5j\omega V_{\text{in}} \rightarrow \frac{dV_{\text{out}}(t)}{dt} + 20V_{\text{out}}(t) = 5 \frac{dV_{\text{in}}(t)}{dt}$

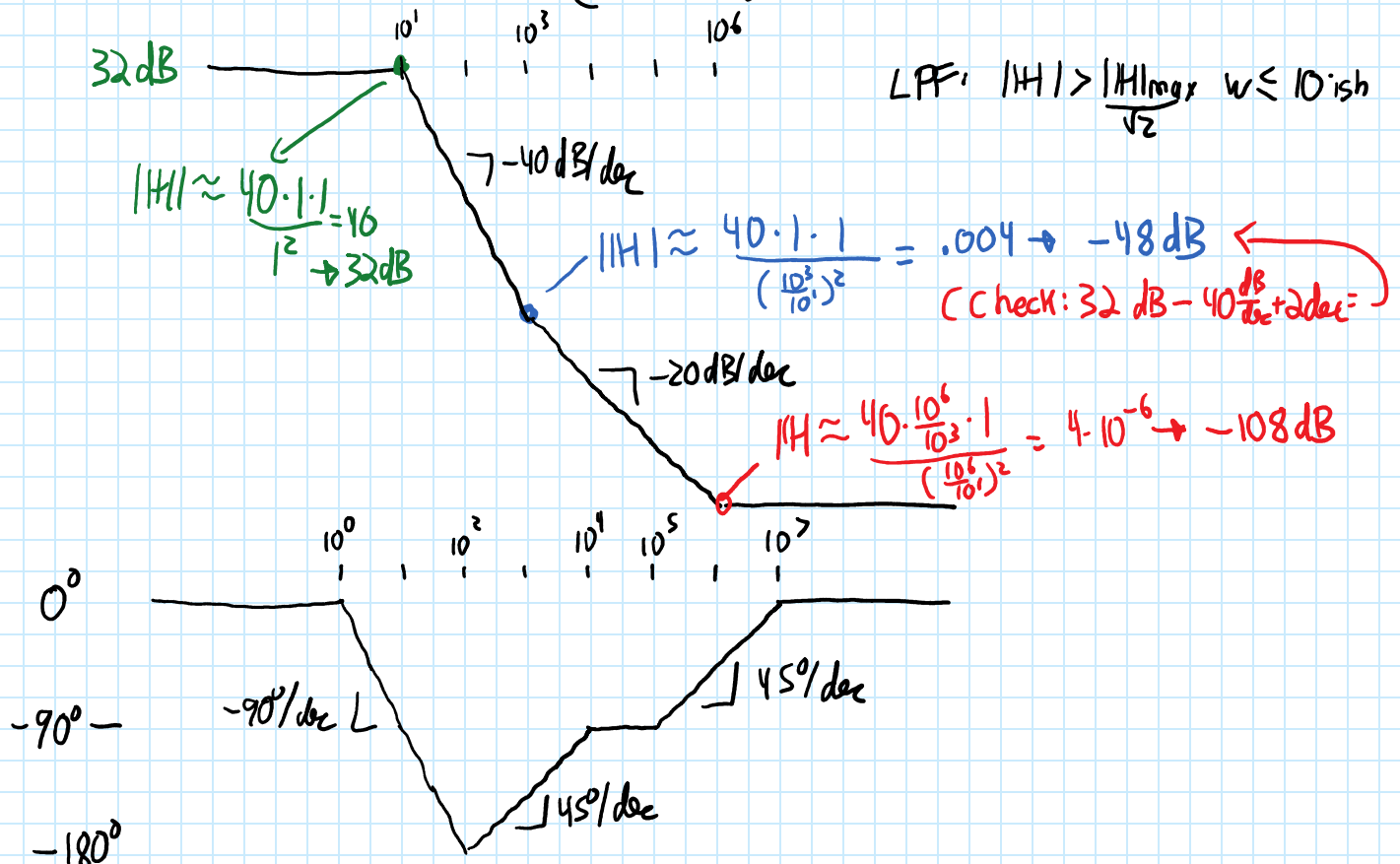(2) $H_2(j\omega) = \frac{40 (1 + j\frac{\omega}{10^3})(1 + j\frac{\omega}{10^6})}{(1 + j\frac{\omega}{10^1})^2}$



(c) LPF, $|H| > \frac{1}{\sqrt{2}} |H|_{\max}$ FOR $\omega < 10^1 \text{ ish}$

$\text{MAX GAIN} = 40 \text{ or } 32 \text{ dB}$

$(2 \cdot 2 \cdot 10 \rightarrow 6 \text{ dB} + 6 \text{ dB} + 20 \text{ dB})$