

Problem I

Monday, April 11, 2022

$$(1) \quad v_1 = L \frac{di_1}{dt} \quad v_2 = Ri_2 \quad i_3 = C \frac{dv_3}{dt}$$

$$(2) \quad E_L = \frac{1}{2} Li^2 \quad E_C = \frac{1}{2} Cv^2$$

$$(3) \quad j\omega L \quad R \quad \frac{1}{j\omega C}$$

(4) current through inductor
voltage across capacitor

Problem II

$$(1) \quad -2 \angle 90^\circ + 5 \angle 0^\circ = 5.385 \angle 21.80^\circ$$

$$\rightarrow 5.385 \cos(22t + 21.80^\circ)$$

$$(2) \quad 5 \angle 30^\circ + 6 \angle 60^\circ = 10.63 \angle 46.40^\circ$$


$$\rightarrow 10.63 \cos(7t + 46.40^\circ)$$

$$(3) \quad V = 5 \angle 0^\circ \quad I = 553.3 \cdot 10^{-6} \angle 51.71^\circ$$

$$Z = \frac{V}{I} = 9037 \angle -51.71^\circ = 5600 - j7093 \, \Omega$$

$$Y = \frac{1}{Z} = 6.857 \cdot 10^{-5} + j8.685 \cdot 10^{-5} \, \text{S}$$

$X < 0$: CAPACITOR:

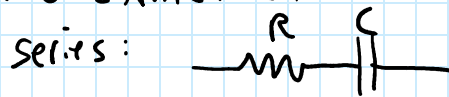

$$Z = R + \frac{1}{j\omega C}$$

$$R = 5600$$

$$\frac{1}{\omega C} = 7093$$

$$C = \frac{1}{7093 \cdot \omega}, \omega = 3, C = 47 \, \mu\text{F}$$



$$Y = \frac{1}{R} + j\omega C$$


$$R = \frac{1}{6.85 \cdot 10^{-5}} = 14590 \, \Omega$$

$$\omega C = 8.685 \cdot 10^{-5}$$

$$C = \frac{8.685 \cdot 10^{-5}}{\omega}, \omega = 3, C = 28.95 \, \mu\text{F}$$


Problem III

$t=0^-$:

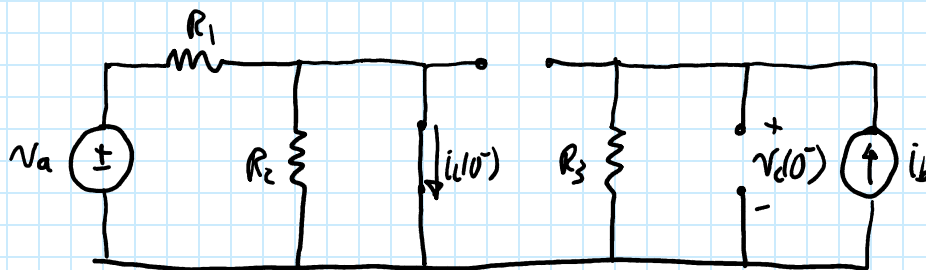

$$v_L(0^-) = 0 \quad \bar{i}_C(0^-) = 0 \quad i_L(0^-) = \frac{v_a}{R_1} \quad v_C(0^-) = R_3 i_b$$

$t=0^+$

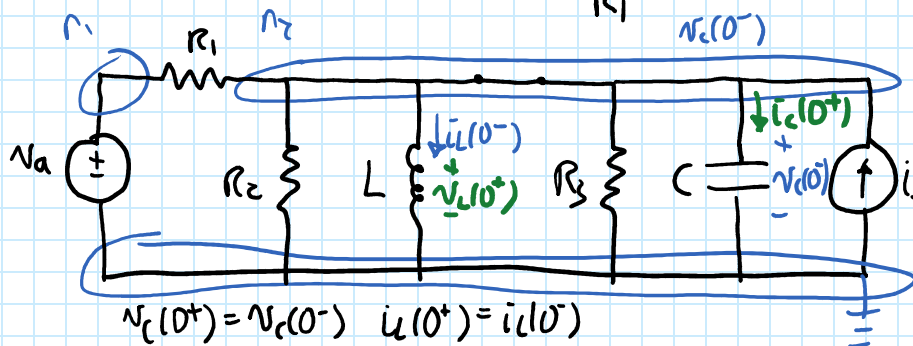


$$v_C(0^+) = v_C(0^-) \quad i_L(0^+) = i_L(0^-)$$

$$v_L(0^+) = v_C(0^-) \quad \text{KCL, n}_2: \frac{v_C(0^-) - v_a}{R_1} + \frac{v_C(0^-)}{R_2} + i_L(0^+) + \frac{v_C(0^-)}{R_3} + \bar{i}_C(0^+) - i_b = 0$$

$$\bar{i}_C(0^+) = \frac{v_a}{R_1} - v_C(0^-) \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + i_b = \frac{v_a}{R_1} - R_3 i_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$\frac{v_a}{R_1}$ $\frac{v_C(0^-)}{R_3}$ (cancels) i_b

$t \rightarrow \infty$

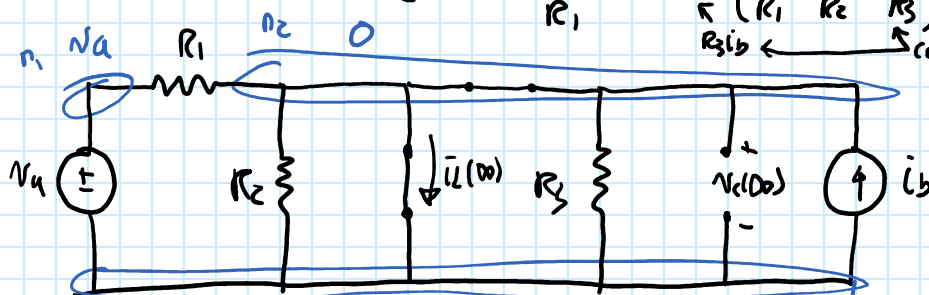

$$v_L(\infty) = 0 \quad \bar{i}_C(\infty) = 0 \quad v_C(\infty) = 0 \quad (\text{inductor shorts})$$

$$\text{KCL, n}_2: \frac{0 - v_a}{R_1} + \bar{i}_L(\infty) - i_b = 0 \quad i_L(\infty) = \frac{v_a}{R_1} + i_b$$

$$v_C(0^-) = R_3 i_b \quad \longrightarrow \quad v_C(0^+) = R_3 i_b$$

$$v_C(\infty) = 0$$

$$\bar{i}_C(0^-) = 0$$

$$\bar{i}_C(0^+) = \frac{v_a}{R_1} - R_3 i_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\bar{i}_C(\infty) = 0$$

$$v_L(0^-) = 0$$

$$v_L(0^+) = R_3 i_b$$

$$v_L(\infty) = 0$$

$$i_L(0^-) = \frac{v_a}{R_1}$$

$$\longrightarrow i_L(0^+) = \frac{v_a}{R_1}$$

$$i_L(\infty) = \frac{v_a}{R_1} + i_b$$


Problem IV

$$4 \frac{dv_o}{dt} + 3v_o = 6$$

normalize to get
 v_o alone


$$\underbrace{\frac{4}{3}}_{\tau} \frac{dv_o}{dt} + \underbrace{v_o}_{v_o(\infty)} = 2 \quad v_o(0) = -8$$

$$\begin{aligned} v_o(t) &= v_{o,f} + (v_{o,i} - v_{o,f}) e^{-(t-t_0)/\tau} \\ &= 2 + (-8 - 2) e^{-t/(4/3)} \\ &= 2 - 10 e^{-t/(4/3)} \end{aligned}$$

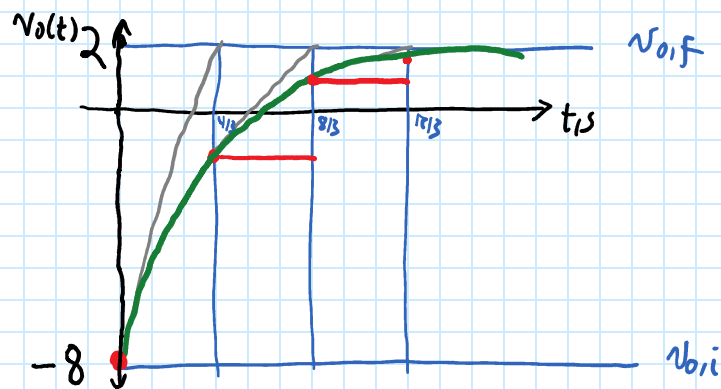

Problem V


(1)

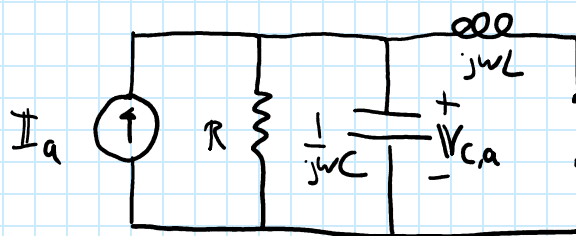

$$V_{C,a} = Z_{eq} I_a \quad H_a = \frac{V_{C,a}}{I_a} = Z_{eq}$$

$$H_a = \frac{1}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} = \frac{j\omega L R}{(j\omega)^2 L R C + (j\omega)L + R}$$

(2)

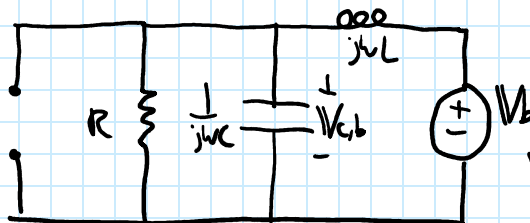

$$Z_{RC} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{j\omega R C + 1}$$

$$V_{C,b} = \frac{V_b Z_{RC}}{j\omega L + Z_{RC}} = \frac{V_b \frac{R}{j\omega R C + 1}}{j\omega L + \frac{R}{j\omega R C + 1}} = \frac{V_b R}{(j\omega)^2 L R C + j\omega L + R}$$


$$H_b = \frac{V_{C,b}}{V_b} = \frac{R}{(j\omega)^2 L R C + j\omega L + R}$$

(3)	ω	I_a	H_a	V_b	H_b	$I_a H_a + V_b H_b$
	0	3	0	4	1	4
	8000	0	N/R	$8\angle -40^\circ$	$1.184\angle -28.26^\circ$	$9.471\angle -68.26^\circ$
	20000	$7.10^3\angle 20^\circ$	$1715\angle -30.96^\circ$	0	N/R	$12.00\angle -10.96^\circ$
	$v_L(t) = 4 + 9.471\cos(8000t - 68.26^\circ) + 12.00\cos(20000t - 10.96^\circ) \text{ V}$					


Problem VI

$$|H| = \frac{200000 (j\omega)^2}{(j\omega + 10)(j\omega + 10000)} = \frac{2 (j\omega)^2}{(1 + j\frac{\omega}{10})(1 + j\frac{\omega}{10000})}$$

(1)

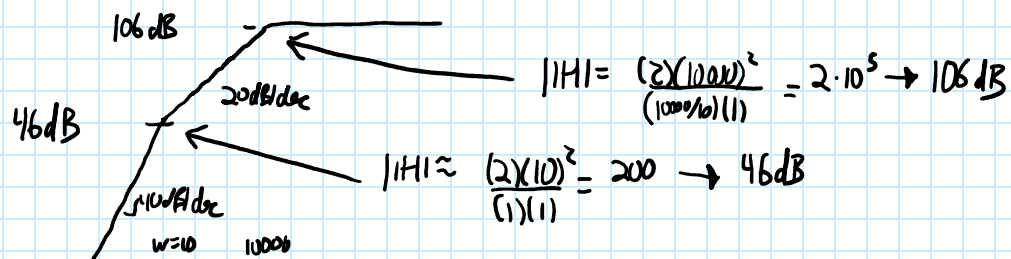

(2)

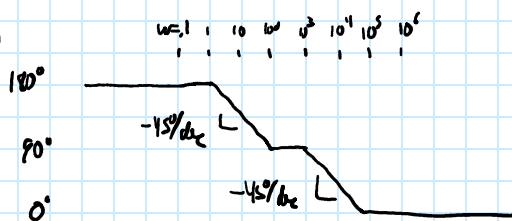

(3) HPF

$$\text{Max Gain} = 200000 \text{ or } 106 \text{ dB}$$

$$\omega_{\text{cutoff}} \approx 10000 \text{ rad/s}$$

(4)

$$\frac{V_{out}}{V_{in}} = \frac{200000 (j\omega)^2}{(j\omega)^2 + (10010)j\omega + 100000}$$

$$((j\omega)^2 + 10010j\omega + 100000)V_{out} = 200000 (j\omega)^2 V_{in}$$

$$\frac{d^2 v_{out}(t)}{dt^2} + 10010 \frac{dv_{out}(t)}{dt} + 100000 v_{out}(t) = 200000 \frac{d^2 v_{in}(t)}{dt^2}$$

Problem VII

- * COMES IN FLAT: NO ZONE ($j\omega$)
- * UP AT 100: $(1 + j\omega/100)$ on top
- * down AT 2000: $(1 + j\omega/2000)$ on bottom
- * double down at $1 \cdot 10^5$ $(1 + j\omega/10^5)^2$ on bottom

$$H = \frac{K(1 + j\omega/100)}{(1 + j\omega/2 \cdot 10^3)(1 + j\omega/10^5)^2}$$

$$H(100) \approx 1000 \quad (60 \text{ dB} \rightarrow 1000)$$

$$H(100) \approx \frac{K \cdot 1}{1 \cdot 1^2} = K \quad K = 1000$$

$$H = \frac{1000(1 + j\omega/100)}{(1 + j\omega/2 \cdot 10^3)(1 + j\omega/10^5)^2} = \frac{2 \cdot 10^{14} (j\omega + 100)}{(j\omega + 2000)(j\omega + 10^5)^2}$$

$$H(2000) \approx \frac{1000 \cdot 2000/100}{1 \cdot 1^2} = 20000 \rightarrow 86 \text{ dB}$$