

## Problem I

$$(1) \quad v_1 = L \frac{di_1}{dt} \quad v_2 = R i_2 \quad i_3 = C \frac{dv_3}{dt}$$

$$(2) \quad \frac{1}{2} L i_1^2 \quad \frac{1}{2} C v_3^2$$

$$(3) \quad j\omega L \quad R \quad \frac{1}{j\omega C}$$

(4) current ... voltage

## Problem II

$$(1) \quad 40 \text{ mH} \parallel 20 \text{ mH} = \frac{40 \cdot 20}{40+20} = \frac{800}{60} = 13\bar{3} \text{ mH} + 90 \text{ mH} = 103\bar{3} \text{ mH}$$

$$(2) \quad C \text{ in parallel add, so } C_{\text{right}} = 600 \text{ nF}$$


$$C \text{ in series add in mverse, so } C_{\text{eff}} = \frac{1}{\frac{1}{200 \text{ nF}} + \frac{1}{800 \text{ nF}} + \frac{1}{600 \text{ nF}}} = 126.3 \text{ nF}$$

(3)

$$Z_{R1L} = 200 + j400 \quad Z_{CR2} = \frac{(-j500)(2000)}{-j500 + 2000} = 485.1 \angle -75.96^\circ$$

$$Z_{R1L} + Z_{CR2} = 325 \angle -12.53^\circ = 317.3 - 70.51 \Omega$$

(4) DCSS

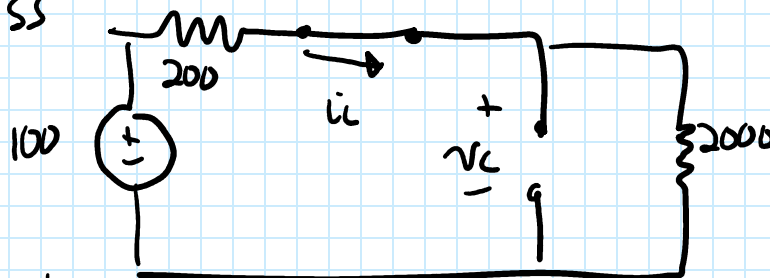

$$i_C = \frac{100}{2200} = 0.04546 \text{ A}$$


$$v_C = \frac{100 \cdot 2000}{2200} = 90.91 \text{ V}$$

$$E = \frac{1}{2} L i^2 = 82.65 \mu\text{J}$$

$$E = \frac{1}{2} C v^2 = 1.653 \text{ mJ}$$

# Problem III

$t < 0$   $n_1$   $\bigcirc$

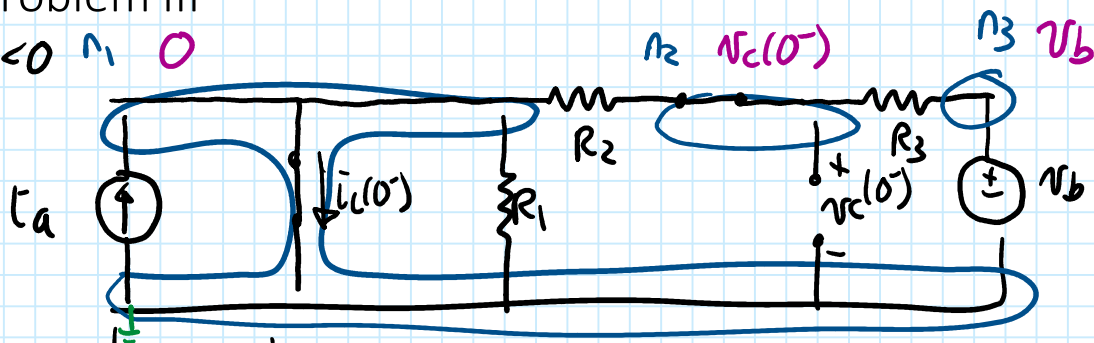


Several ways to solve. NVM?

$$KCL, n_2: \frac{v_c(0^-) - 0}{R_2} + \frac{v_c(0^-) - v_b}{R_3} = 0 \quad v_c(0^-) = \frac{R_2 v_b}{R_2 + R_3}$$

$$KCL, n_1: -i_a + i_L(0^-) + 0 - \frac{v_c(0^-)}{R_2} = 0$$

$$i_L(0^-) = i_a + \frac{R_2 v_b}{R_2(R_2 + R_3)} = i_a + \frac{v_b}{R_2 + R_3}$$

$$v_L(0^-) = 0 \quad i_c(0^-) = 0$$

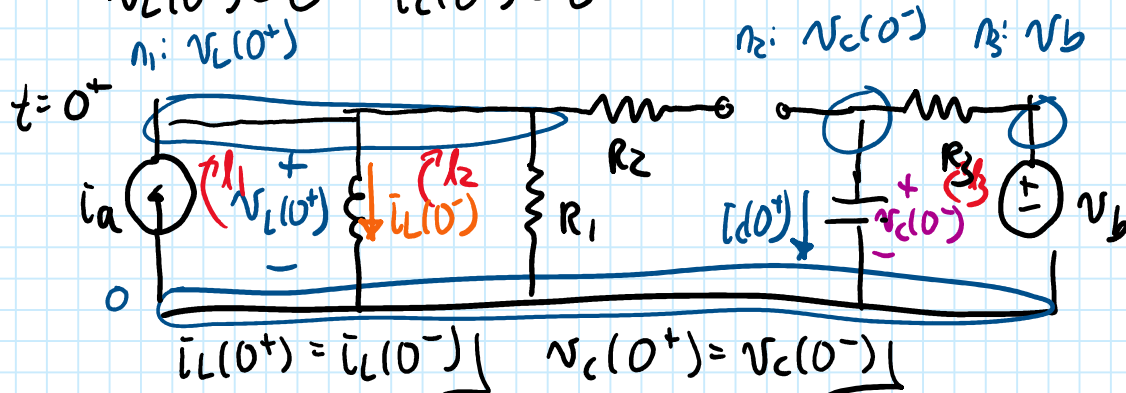


$$KCL, n_1: -i_a + i_L(0^+) + \frac{v_L(0^+)}{R_1} = 0$$

$$v_L(0^+) = R_1(i_a - i_L(0^+)) = R_1(i_a - i_a - \frac{v_b}{R_2 + R_3}) = -\frac{R_1 v_b}{R_2 + R_3}$$

$$KVL, n_3: -v_c(0^+) - R_3 i_c(0^+) + v_b = 0$$

$$i_c(0^+) = \frac{v_b - v_c(0^+)}{R_3} = \frac{v_b - \frac{R_2 v_b}{R_2 + R_3}}{R_3} = \frac{v_b}{R_2 + R_3}$$

$t \rightarrow \infty$

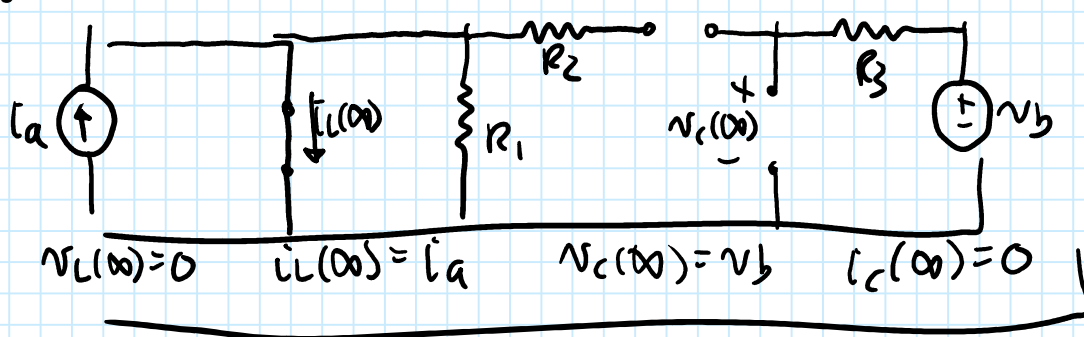

# Problem IV


$$7 \frac{di_o}{dt} + 2i_o = -10 \text{ mA}$$

$$3.5 \frac{di_o}{dt} + i_o = -5 \text{ mA} \quad i_o(0) = 4 \text{ mA}$$

$$\tau = 3.5 \quad i_o(0) = 4 \text{ mA} \quad i_o(\infty) = -5 \text{ mA}$$

$$i_o(t) = -5 + (4 - (-5))e^{-t/3.5} \text{ mA}$$

$$= -5 + 9e^{-t/3.5} \text{ mA}$$

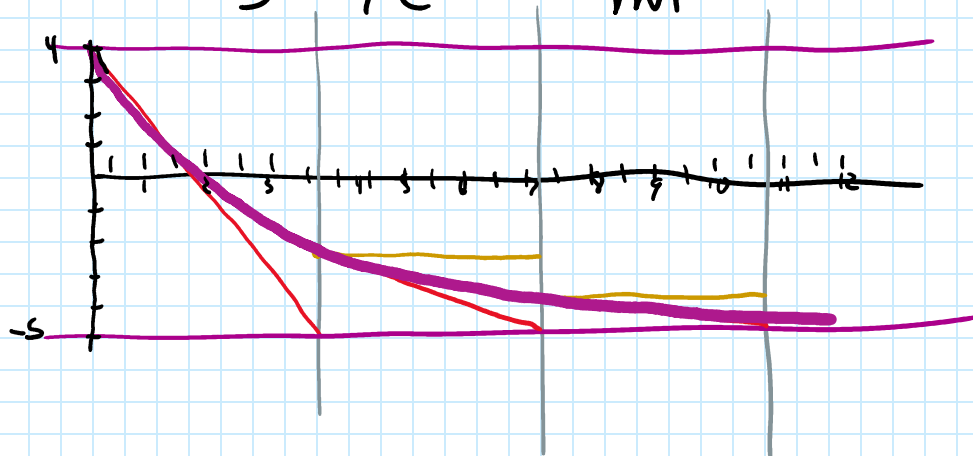

# Problem V

$$H = \frac{10}{j\omega + 5}$$

$$\frac{X_{out}}{X_{in}} = \frac{10}{j\omega + 5}$$

$$(j\omega + 5)X_{out} = 10X_{in}$$

$$\frac{dX_{out}(t)}{dt} + 5X_{out}(t) = 10X_{in}(t)$$


$$X_{in}(t) = 1 + 3\cos(5t) + 7\cos(9t + 20^\circ)$$

$\omega$	$X_{in}$	$H(j\omega)$	$X_{in} \cdot H(j\omega)$
0	1	$2\angle 0^\circ$	$2\angle 0^\circ$
5	$3\angle 0^\circ$	$\frac{10}{j5+5} = 1.414\angle -45^\circ$	$4.243\angle -45^\circ$
9	$7\angle 20^\circ$	$\frac{10}{j9+5} = 0.9713\angle -60.95^\circ$	$6.8\angle -40.95^\circ$

$$X_{out}(t) = 2 + 4.243\cos(5t - 45^\circ) + 6.8\cos(9t - 40.95^\circ)$$

$$\text{or } + 6.8\sin(9t + 49.05^\circ)$$


# Problem VI

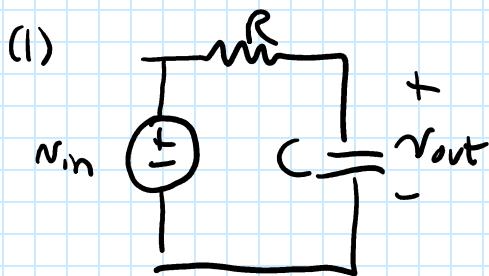

$$H = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\frac{\omega}{2000}}$$

$$\omega_{\text{cutoff}} = \frac{1}{RC} = 2000$$
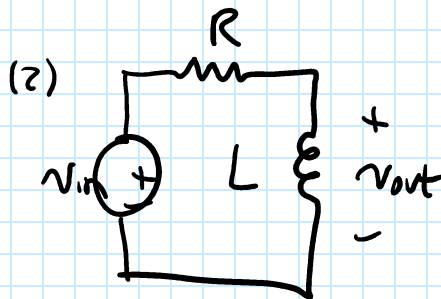
$$C = \frac{1}{(2000)(1000)} = 500 \text{ nF}$$



$$H = \frac{j\omega L}{R + j\omega L} = \frac{j\omega L/R}{1 + j\omega L/R} = \frac{j\omega/5000}{1 + j\omega/5000}$$

$$\omega_{\text{cutoff}} = \frac{R}{L} = 5000$$

$$L = \frac{R}{5000} = \frac{2000}{5000} = 0.4 \text{ H}$$

# Problem VII

$$(1) \quad x(t) = 2r(t) - 4u(t-1) - 2r(t-2)$$

$$(2) \quad h(t) = 2u(t) - 2u(t-3)$$

$$(3) \quad x(t) * h(t) =$$

$$\rightarrow \underbrace{4g(t)}_{\text{red}} - \underbrace{8r(t-1)}_{\text{green}} - \underbrace{4g(t-2)}_{\text{blue}}$$

$$\rightarrow \underbrace{-4g(t-3)}_{\text{purple}} + \underbrace{8r(t-4)}_{\text{orange}} + \underbrace{4g(t-5)}_{\text{yellow}}$$

$$(4) \quad t < 0: \quad 0$$

$$0 < t < 1: \quad \underbrace{4g(t)}_{\text{red}} = 4 \left( \frac{1}{2} t^2 \right) = 2t^2$$

$$1 < t < 2 \quad 2t^2 - 8r(t-1) = 2t^2 - 8(t-1) = 2t^2 - 8t + 8$$

$$2 < t < 3 \quad 2t^2 - 8t + 8 - 4 \left( \frac{1}{2} (t^2 - 4t + 4) \right) = 2t^2 - 8t + 8 - 2t^2 + 8t - 8 = 0$$

$$3 < t < 4 \quad 0 - 4g(t-3) = -4 \left( \frac{1}{2} (t^2 - 6t + 9) \right) = -2t^2 + 12t - 18$$

$$4 < t < 5 \quad -2t^2 + 12t - 18 + 8r(t-4) = -2t^2 + 12t - 18 + 8t - 32 = -2t^2 + 20t - 50$$

$$t > 5 \quad -2t^2 + 20t - 50 + 4 \left( \frac{1}{2} (t^2 - 10t + 25) \right)$$

$$-2t^2 + 20t - 50 + 2t^2 - 20t + 50 = 0$$

# Oh, Canada!

```

> restart
> u := t-Heaviside(t) :
> r := t-t·u(t) :
> x := t-2·r(t) - 4·u(t-1) - 2·r(t-2) :
> h := t-2·u(t) - 2·u(t-3) :
> y := t-int(x(tau)·h(t-tau),tau=-infinity..infinity) :
> expand(y(t))

```

```

> plot([x(t),h(t),y(t)],t=-1..5)

```

$$\begin{cases} 0 & t \leq 0 \\ 2t^2 & 0 < t \leq 1 \\ 2t^2 - 8t + 8 & 1 < t \leq 2 \\ 0 & 2 < t \leq 3 \\ -2t^2 + 12t - 18 & 3 < t \leq 4 \\ -2t^2 + 20t - 50 & 4 < t \leq 5 \\ 0 & 5 < t \end{cases}$$

