

Homework 5: Reactive Elements

Introduction

The problems for this week focus on reactive elements and DC steady state.

Problems

Connect

- (1) A&S 6.6.
- (2) A&S 6.8.
- (3) A&S 6.17.
- (4) A&S 6.46.
- (5) A&S 6.48.
- (6) A&S 6.55.
- (7) Based on A&S 6.64. In addition to what is asked on Connect, find all the following:

$$\begin{array}{lll} i_L(0^-) & i_L(0^+) & \lim_{t \rightarrow \infty} i_L(t) \\ v_L(0^-) & v_L(0^+) & \lim_{t \rightarrow \infty} v_L(t) \end{array}$$

You will not be required to turn those items in but do need to know how to find them.

Sakai

None

On your own: Complex Numbers

Learn how to make your calculator do problems like this quickly. Also, find your results in *both* rectangular and polar form. There is a Pundit Page on “Calculator Tips” at: http://pundit.pratt.duke.edu/wiki/Calculator_Tips; the section on how to use the Casio fx-991EX “CLASSWIZ” is underway.

- A&S 9.8.
- A&S 9.9.
- A&S 9.12.
- A&S 9.13.
- A&S 9.14.