

Homework 11: Operational Amplifiers

Introduction

The problems for this assignment focus on operational amplifiers and on using Laplace transforms with them.

Problems

Connect

- (1) **A&S 5.5.** This problem is meant to show you how good the ideal op amp assumptions and the assertions are.
- (2) **A&S 5.24.** There will be two equations with two unknowns here.
- (3) **A&S 5.32.** Remember that the op amp output voltage is not impacted by what happens downstream - find that voltage first and then figure out what that means for the current.
- (4) **A&S 5.59.**
- (5) **A&S 5.71.** You will want to solve this “modularly” - that is, get the output for the left-most op amps first, then use those results to get the total.
- (6) **A&S 14.60.**
- (7) **A&S 14.63.** Section 14.8 is helpful here.
- (8) **A&S 14.64.**
- (9) **A&S 14.67.** Section 14.8 is helpful here. Also, $\text{Hz} \neq \text{rad/s}$.
- (10) **A&S 16.100.**
- (11) **A&S 16.101.** Note that the element types are given to you (elements 1 and 3 are capacitors and element 2 is a resistor; the admittance \mathbb{Y} is given primarily because the feedback path has elements in parallel and you can add parallel admittances).

Sakai

None for this assignment.

Comments

- (1) For most of these op amp problems, you could use the basic configurations in class. Note that is not always the case - for example, Problems 5.60 and 5.62 (among many others that you are not doing) have structures that do not neatly fit into a combination of inverting / non-inverting / summation / difference amplifiers.
- (2) On the other hand, sometimes complicated circuits can be decomposed into modular parts. Problem 5.66, for example, is a combination of an inverting amplifier (the middle part of the circuit) and a summation amplifier with three source / resistor combinations.